

Final Assignment



BRAC University

Semester: Spring 2023

Course No: CSE251


Course Title: Electronic Devices and Circuits

Student IDs:


Set-1

(i)

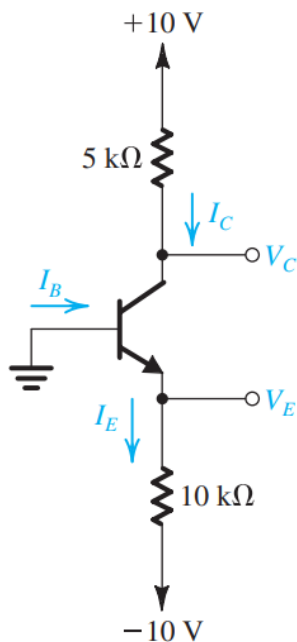In the circuit shown in Fig. the voltage at the emitter was measured and found to be -0.7 V .
If $\beta = 50$, find I_E , I_B , I_C , and V_C .



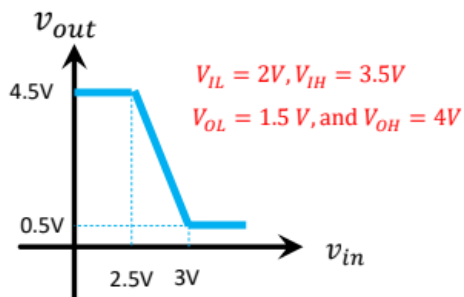(ii) Consider the circuit shown below. Does it follow the Static Discipline?
Calculate the noise margins NM_0 and NM_1 .



Set-2

Consider an NMOS transistor fabricated with $L = 0.18 \mu\text{m}$ and $W = 2 \mu\text{m}$. The process technology is specified to have $k'_n = 387 \mu\text{A/V}^2$, and $V_T = 0.5 \text{ V}$. Find V_{GS} and V_{DS} that result in the MOSFET operating at the edge of the saturation region with $I_{DS} = 100 \mu\text{A}$. If V_{GS} is kept constant, find V_{DS} that results in $I_D = 50 \mu\text{A}$.

For MOSFET

$$k = k'_n \frac{W}{L}$$

$$I_D = 0, \text{ if } V_{GS} < V_T$$

$$I_D = k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right], \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} < (V_{GS} - V_T)$$

$$I_D = \frac{1}{2} k (V_{GS} - V_T)^2, \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} \geq (V_{GS} - V_T)$$

Set-3

(i) Draw the I-V graph of a **MOSFET**. Identify all the regions. [You have to draw for at least three V_{GS} values and mark V_{ov} on the graph.]

(ii) Draw the I-V graph of a **BJT**. Identify all the regions. [You have to draw for at least three I_B values on the graph.]