

Assignment 2



BRAC University

Semester: Spring 2023


Course No: CSE251

Course Title: Electronic Devices and Circuits

Full Marks: 100

Deadline: **2 March 2023**

1.

 

(i) **Draw** the i - V graph of the circuit drawn above. Clearly mention the coordinates of x and y -intersecting points on the graph *[Free-hand drawing is sufficient]*.

(ii) What happens when the resistance becomes (a) **100kΩ**, (b) **200kΩ** instead of **50 kΩ**? **Plot** these cases on the graph and explain the result.

[10+10]

2. Analyze the circuit shown below. Assume all the diodes to be ideal.

Part a:

(ii) Assuming w , x , y , z are boolean variables, **analyze** the circuit to find an expression of ckt-1 (the dotted ... rectangle) in terms of w and x , and an expression of ckt-2 (the dashed - - - rectangle) in terms of y and z .

[5+5]

(b) **Analyze** the circuit again to find an expression of f in terms of w , x , y , z . Use results from (a).


[5]

Part b: Jawad has created a new ride-sharing app: **Juber**. When you request a Juber ride, Juber's algorithm generates 4 signals to determine whether it will be forwarded to a rider. (1) Signal F determines if the rider is free. (2) Signal R determines if the rider is

within close proximity. (3) Signal G determines if the rider has a good rating. (4) Signal N determines if the rider is new. If both conditions 1 and 2 are satisfied, and either condition 3 or condition 4 are satisfied, the request will be connected.

(c) Deduce the logic function using boolean signals F, R, G, and N to implement Juber's algorithm. [10]

 (d) Design a circuit using ideal diode logic gates to implement this function. [15]




3. Find the values of I and V in the circuit shown below for the following cases:

(i) Assuming the diodes to be ideal.

(ii) Assuming the diodes to be non-ideal [Hints: use constant voltage drop model with $V_{D0}=0.7\text{ V}$].

 (iii) Assuming the diodes to be non-ideal and use $5\text{ k}\Omega$ instead of $10\text{ k}\Omega$ [Hints: use constant voltage drop model with $V_{D0}=0.7\text{ V}$]. [8×3=24]



4. Consider the circuit shown in the following Figure. The cut-in voltage of each diode is $V_{D0} = 0.7 \text{ V}$.

Let $v_1 = (5 + \text{last digit of your ID} \times 10^{-2}) \text{ V}$. Assume both diodes are conducting. Is this a correct assumption? Why or why not? Determine I_{R1} , I_{D1} , I_{D2} , and v_O (if necessary, modify the assumption and **calculate the values for the correct one**).

[16]

