

Assignment 3



BRAC University

Semester: Spring 2023

Course No: CSE251



Course Title: Electronic Devices and Circuits

Full Marks: $10 \times 4 \times 2.5 = 100$ [Bonus: 15]

Deadline: **8 April 2023**

Note: The formulas for a MOSFET are given in Ques 2.

1.

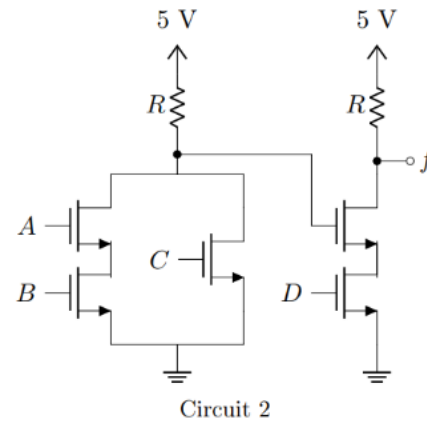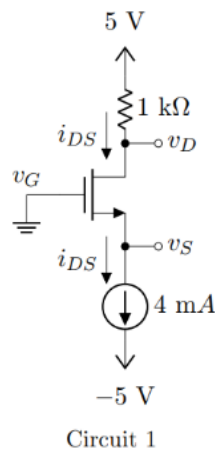

Part a: Refer to the **Circuit 1** above. For the MOSFET, $V_T = 1\text{ V}$ and $k = k'_n \frac{W}{L} = 4\text{ mA/V}^2$.


- (a) **Identify** the value of the gate voltage v_G and the drain-source current i_{DS} . [0.5+0.5]
- (b) **Calculate** the value of the drain voltage v_D using the $1\text{ k}\Omega$ resistor. [1]
- (c) **Analyze** the circuit to find v_S . Here, **use** the Method of Assumed State. You must **validate** your assumptions. [Hint: assume $v_S = x$] [3+2]

Part b: Analyze the **Circuit 2** above to find f in terms of *boolean* inputs A , B , C , and D . [3]

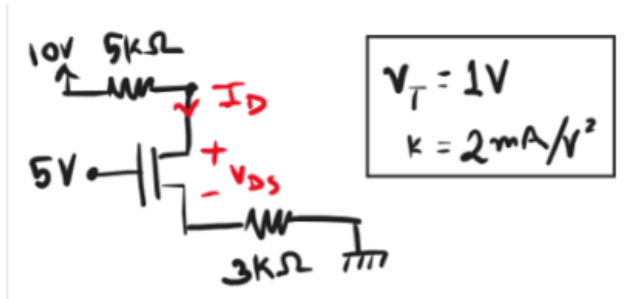2.

Analyze the following circuit to find the values of I_D and V_{DS} **using** the Method of Assumed State. You must **validate** your assumptions.

Hint: Use I_D as unknown x . Use Ohm's law to represent V_D and V_S in terms of x .



For MOSFET


$$k = k'_n \frac{W}{L}$$

$$I_D = 0, \text{ if } V_{GS} < V_T$$

$$I_D = k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right], \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} < (V_{GS} - V_T)$$

$$I_D = \frac{1}{2} k (V_{GS} - V_T)^2, \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} \geq (V_{GS} - V_T)$$

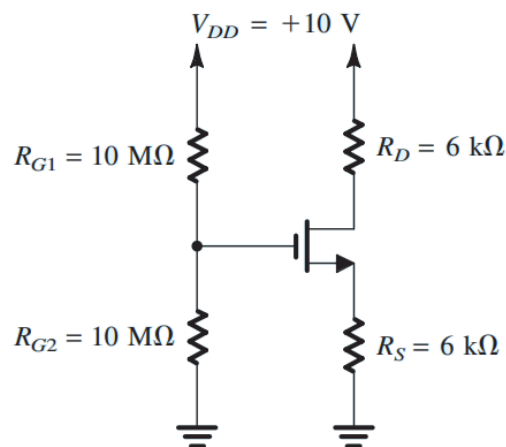3. Analyze the circuit shown in the following Figure to determine the voltages at all nodes and the currents through all branches. Let $V_T = 1 \text{ V}$ and $k'_n(W/L) = 1 \text{ mA/V}^2$. **[10]**
[Hints: current at the gate terminal is zero for a MOSFET].



4. Implement using MOSFETs:

[10]

(a) $f = (A + B)C$

(b) $f = (\overline{A}B + CD)$

(c) $f = AB + A + CD$ (with and without simplifying the logic)

BONUS: An NMOS transistor is operating at the edge of saturation with an overdrive voltage V_{ov} and a drain current I_D . If V_{ov} is doubled, and we must maintain operation at the edge of saturation, what should V_{DS} be changed to? **Find** the value of drain current results. Does changing V_{ov} change the process parameter k ? [0.5+3+1.5]