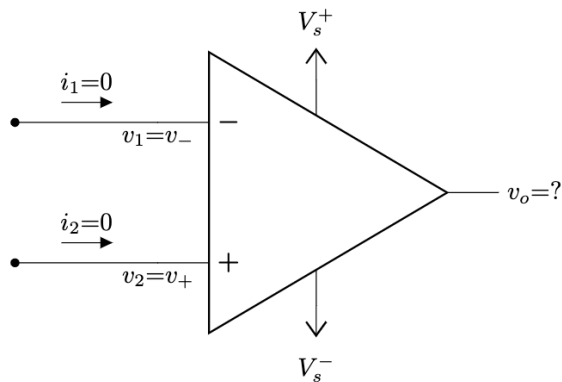


Lecture 5


Op Amp – Part 3

Solving Circuit with Ideal Op Amp + NF

- For ideal op-amp
 - Infinite input resistance, $R_i = \infty = \text{open circuit}$
 - Zero output resistance, $R_o = 0 = \text{short circuit}$
 - $i_i = 0$ and $i_+ = 0$
- **When there is negative feedback**, For ideal A as is infinitely high, for a finite output voltage v_o , $\frac{v_o}{A} = v_d = 0 \Rightarrow v_+ = v_-$. This is called **virtual short circuit**
- Because of these, solving ideal op-amp circuit with negative feedback is very simple



Review – Inverting Amplifier

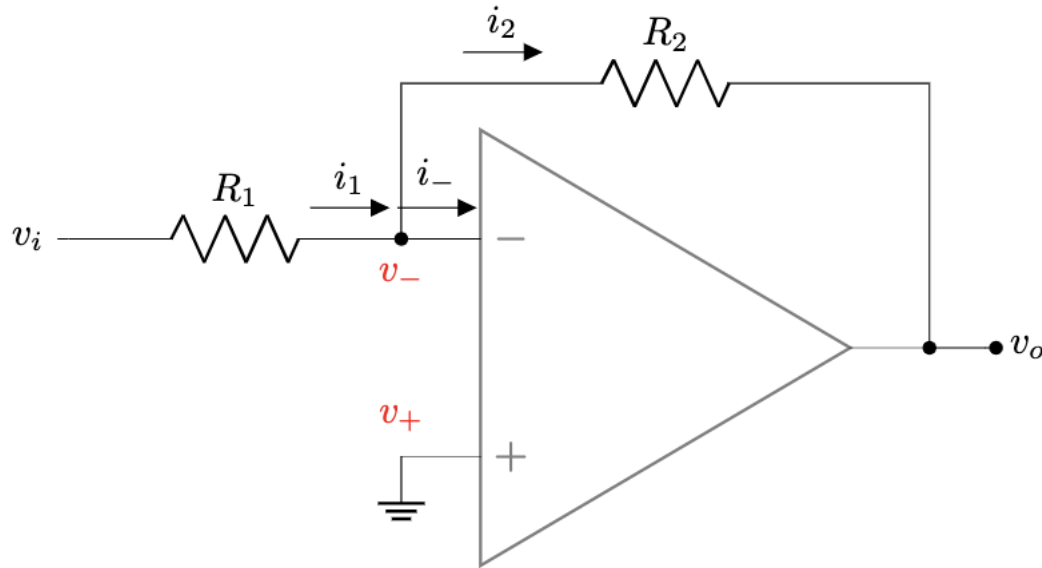

Since v_+ is connected to ground, $v_+ = 0V$

Since there is negative feedback, from virtual short, $v_- = v_+ = 0V$

From Ohm's law for $R_1 \Rightarrow i_1 = \frac{v_i - 0V}{R_1} = v_i/R_1$


Since ideal op-amp, $i_- = i_+ = 0$

From KCL at v_- , $i_1 = i_- + i_2 \Rightarrow i_1 = i_2 = v_i/R_1$

From Ohm's law for $R_2 \Rightarrow i_2 = \frac{v_- - v_o}{R_2} = \frac{v_i}{R_1} \Rightarrow v_o = -i_2 \times R_2 \Rightarrow v_o = -\frac{R_2}{R_1} v_i$ [ANS]

$$\text{Gain} = -\frac{R_2}{R_1}$$

Example – Inverting Amplifier

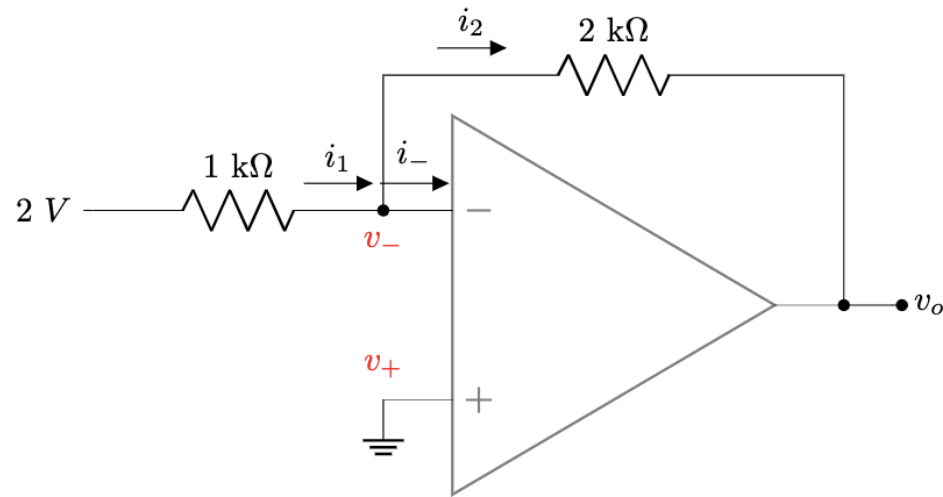

Since v_+ is connected to ground, $v_+ = 0V$

Since there is negative feedback, from virtual short, $v_- = v_+ = 0V$

From Ohm's law for 1 kΩ $\Rightarrow i_1 = \frac{2V - 0V}{1 \text{ k}\Omega} = 2mA$



$$\text{Gain} = -\frac{4V}{2V} = -2 \text{ (hence **inverting**)}$$

Since ideal op-amp, $i_- = i_+ = 0$

From KCL at v_- , $i_1 = i_- + i_2 \Rightarrow i_1 = i_2 = 2 \text{ mA}$

From Ohm's law for 2 kΩ $\Rightarrow i_2 = \frac{v_- - v_o}{2 \text{ k}\Omega} = 2mA \Rightarrow v_o = -i_2 \times 2 = -4V$ [ANS]

Example

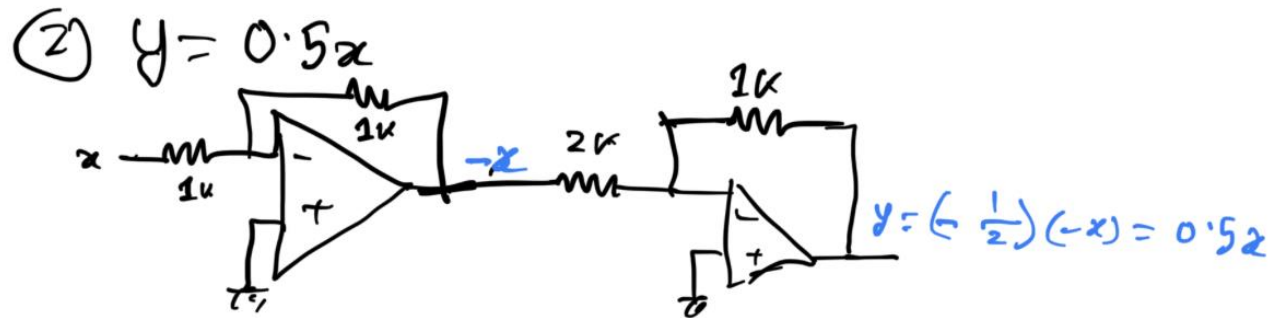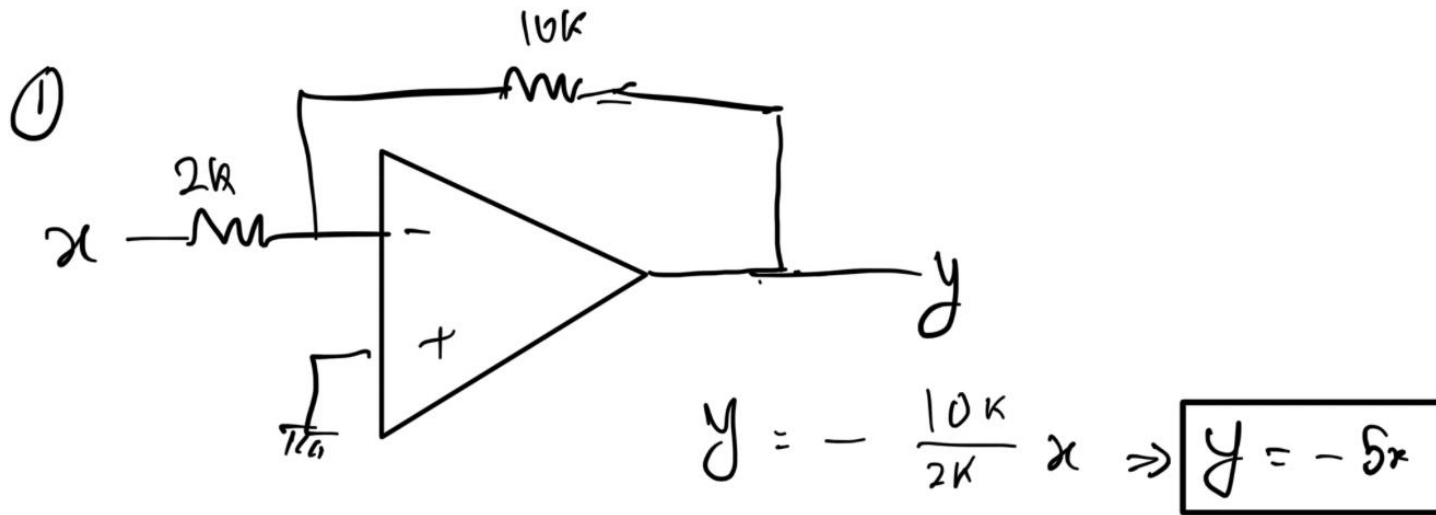

Inverting Adder

Consider v_1 first, and deactivate other (v_2, v_3, v_4) sources.

It is nothing but a non-inverting amplifier.

$$\text{So, } v_{o1} = -\frac{R_f}{R_1} v_1$$

Similarly, if we active one source and deactivate others, we will get:

$$v_{o2} = -\frac{R_f}{R_2} v_2, v_{o3} = -\frac{R_f}{R_3} v_3, v_{o4} = -\frac{R_f}{R_4} v_4$$


Now, using **superposition principle**,

$$v_o = v_{o1} + v_{o2} + v_{o3} + v_{o4}$$

$$\text{So, } v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 - \frac{R_f}{R_3} v_3 - \frac{R_f}{R_4} v_4$$

$$\text{Or, } v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 + \frac{R_f}{R_4} v_4\right)$$

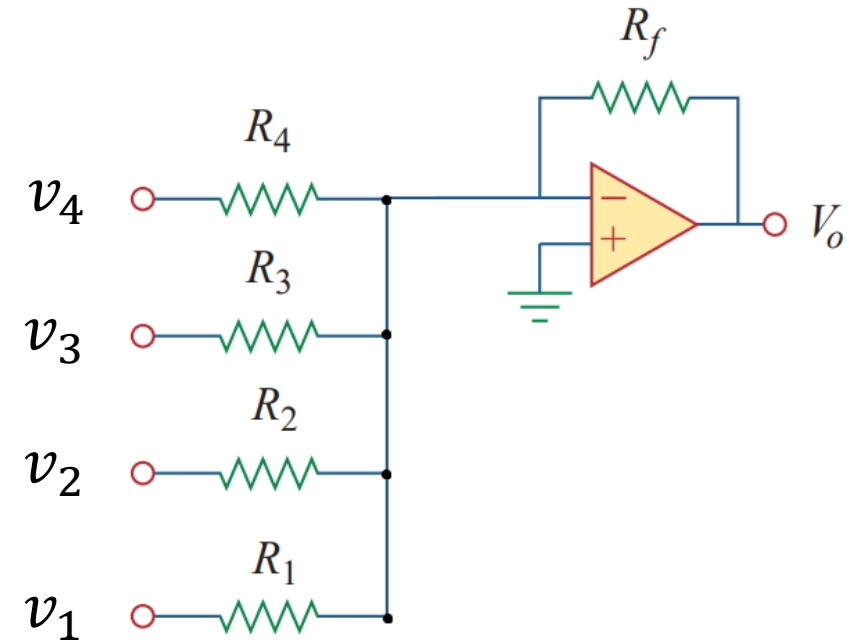We can use this circuit to add any 'n' number of inputs!



Example

Implement the following function using op-amps:


$$v_0 = -(v_1 + 0.5v_2 + v_3)$$

Solution:

Here, $R_f/R_1 = 1$, $R_f/R_2 = 0.5$, $R_f/R_3 = 1$

If $R_f = 1 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_3 = 1 \text{ k}\Omega$

Op Amp as Differentiator

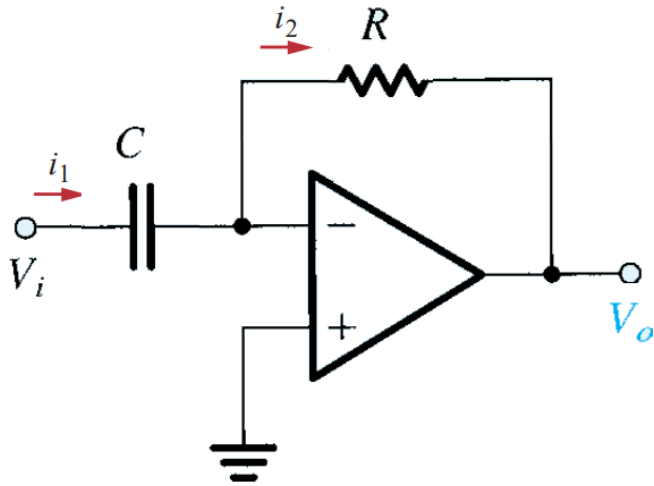

Since v_+ is connected to ground, $v_+ = 0V$

Since there is negative feedback, from virtual short, $v_- = v_+ = 0V$


For the capacitor C , $\Rightarrow i_1 = C \frac{dv_C}{dt} = C \frac{d(v_i - v_-)}{dt} = C \frac{dv_i}{dt}$

From Ohm's law for $R \Rightarrow i_2 = \frac{v_- - v_o}{R} = -\frac{v_o}{R}$

Since ideal op-amp, $i_- = i_+ = 0$, so $i_1 = i_2$

$$\Rightarrow -\frac{v_o}{R} = C \frac{dv_i}{dt} \Rightarrow v_o = -RC \frac{dv_i}{dt} \text{ [Ans.]}$$

Review – Capacitor

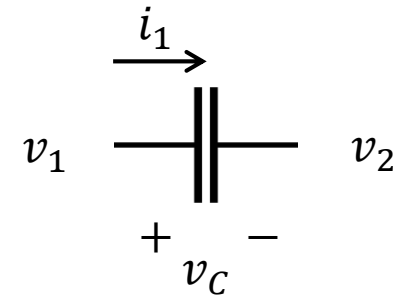

$$i_1 = C \frac{dv_C}{dt} = C \frac{d(v_1 - v_2)}{dt}$$

Op Amp as Integrator

Since v_+ is connected to ground, $v_+ = 0V$

Since there is negative feedback, from virtual short, $v_- = v_+ = 0V$

From Ohm's law for $R \Rightarrow i_1 = \frac{v_i - v_-}{R} = \frac{v_i}{R}$


For the capacitor C , $\Rightarrow i_2 = C \frac{dv_C}{dt} = C \frac{d(v_- - v_o)}{dt} = -C \frac{dv_o}{dt}$

Since ideal op-amp, $i_- = i_+ = 0$, so $i_1 = i_2$

$$\Rightarrow \frac{v_i}{R} = -C \frac{dv_o}{dt}$$


$$= -RC \frac{dv_o}{dt}$$
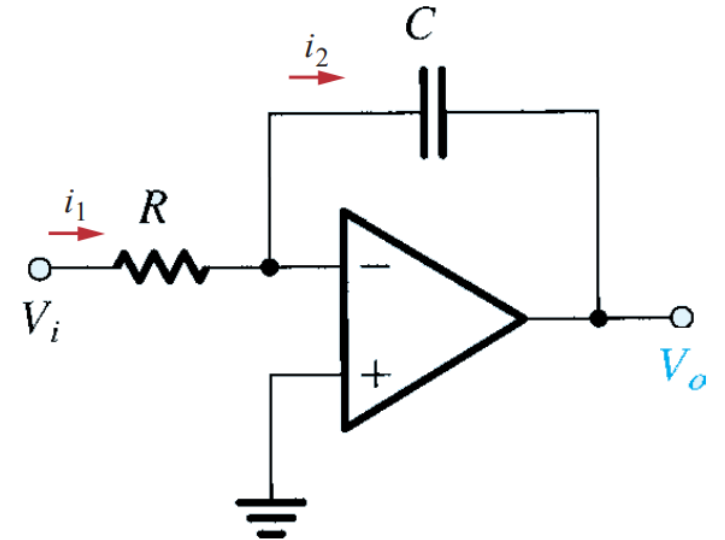
$$\Rightarrow v_o = -\frac{1}{RC} \int v_i dt$$



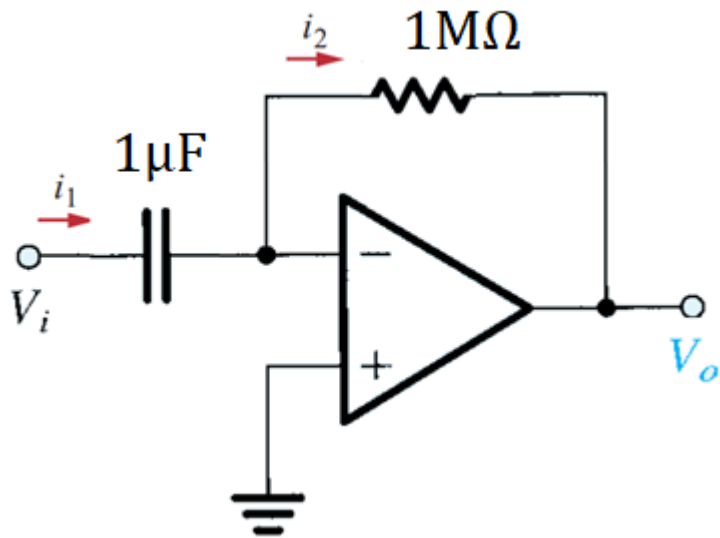Example

Observe the following Figure. If $v_i = 5\sin 6t$, Find the value of v_o .




Solution:

This is a **differentiator**.

$$\text{So, } v_o = -RC \frac{dv_i}{dt} = -1 \times 10^6 \times 1 \times 10^{-6} \times \frac{d(5\sin 6t)}{dt}$$
$$\Rightarrow v_o = -1 \times (5 \times 6 \cos 6t) = -30 \cos 6t \text{ [Ans.]}$$

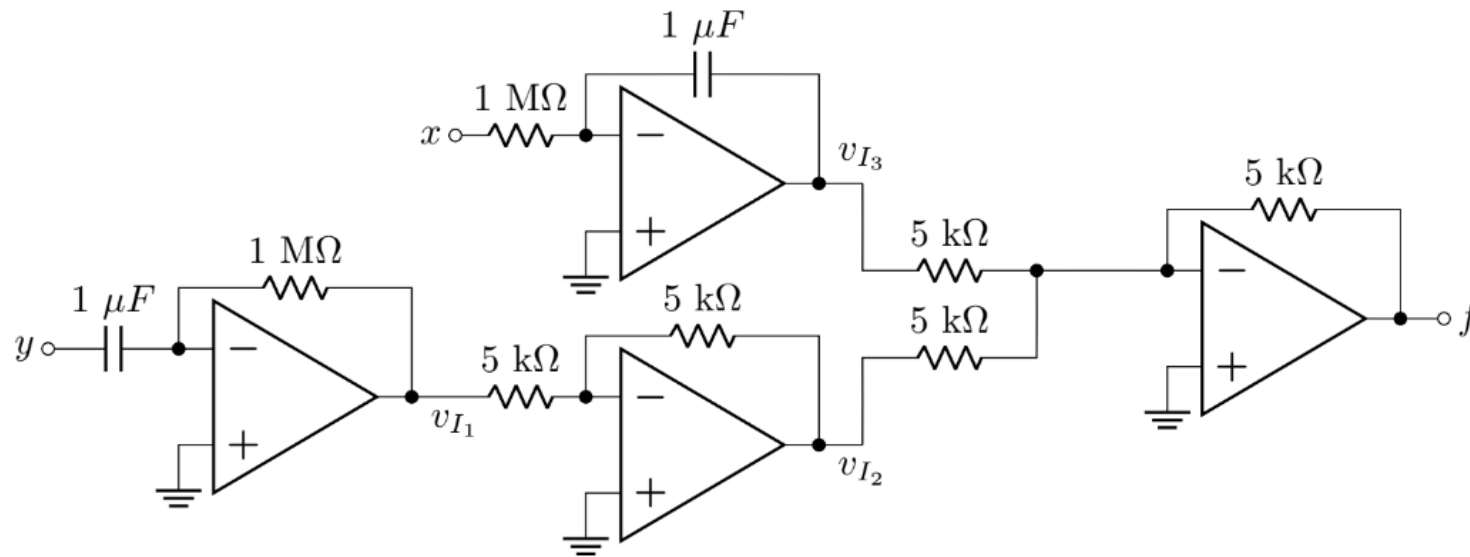Example

Analyze the circuit below to **find** an expression of f in terms of inputs x and y .



Solution:

$$v_{f1} = -\frac{dy}{dt}; v_{f2} = -\frac{1}{RC} \int x\ dt; v_{f3} = -v_{f1} = \frac{dy}{dt}; v_o = -(v_{f2} + v_{f3})$$

Op Amp as Comparator

- A comparator compares two voltages to determine which is larger.


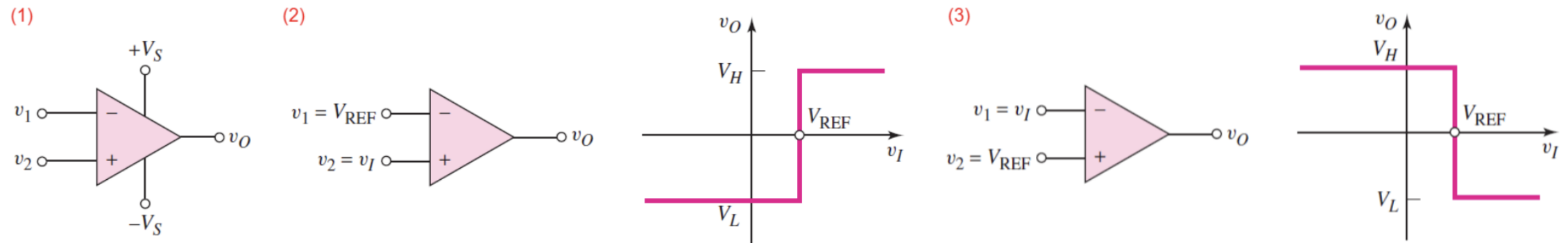


Figure 2: (1) Op-Amp Comparator (2) Noninverting Circuit (3) Inverting Circuit


What if noise enters the system?

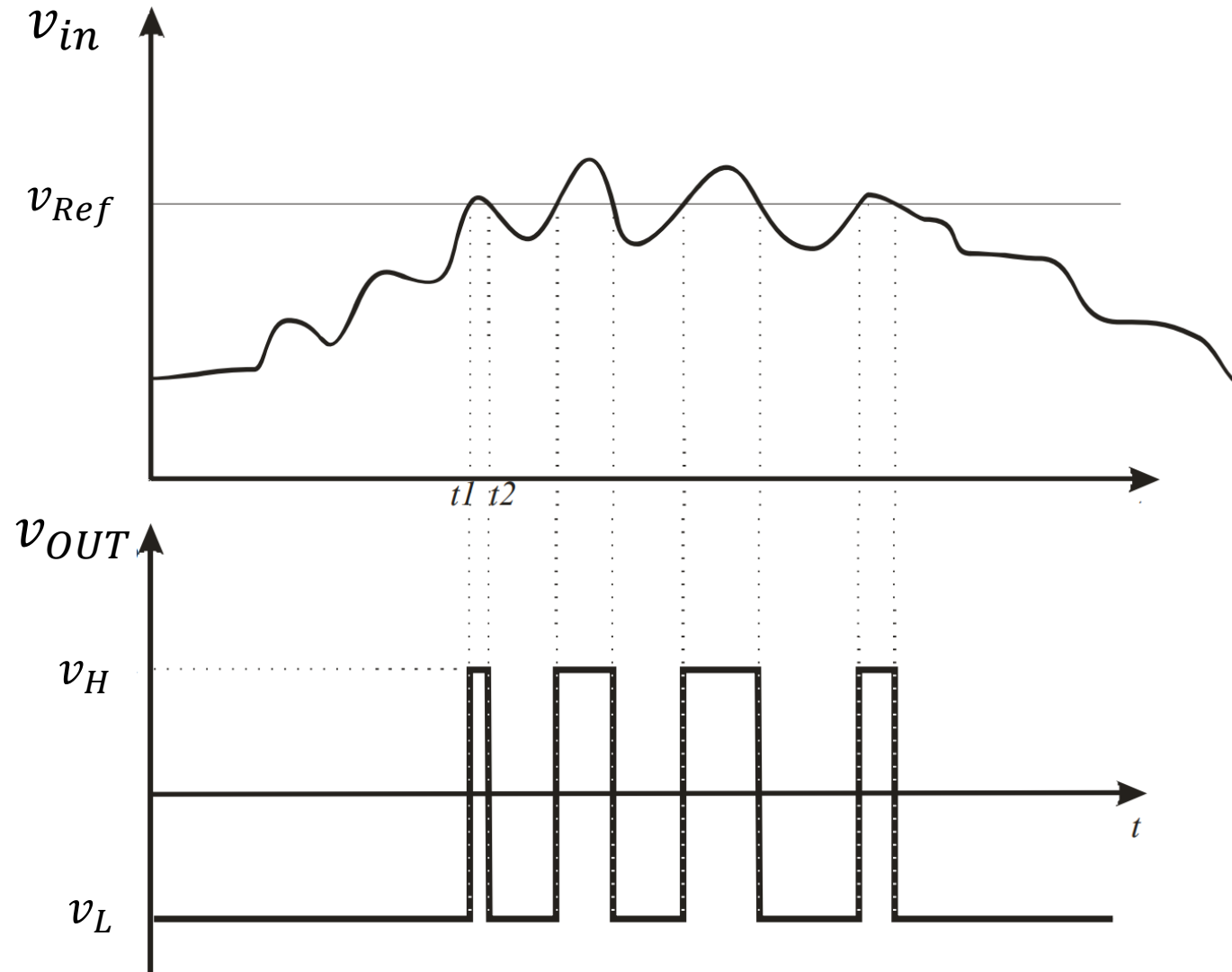- As v_{in} exceeds v_{Ref} , the voltage at the output of the comparator (v_{OUT}) switches from v_L to v_H
- We want to make the system immune to noise.



Introducing double thresholds (v_{TH} and v_{TL})

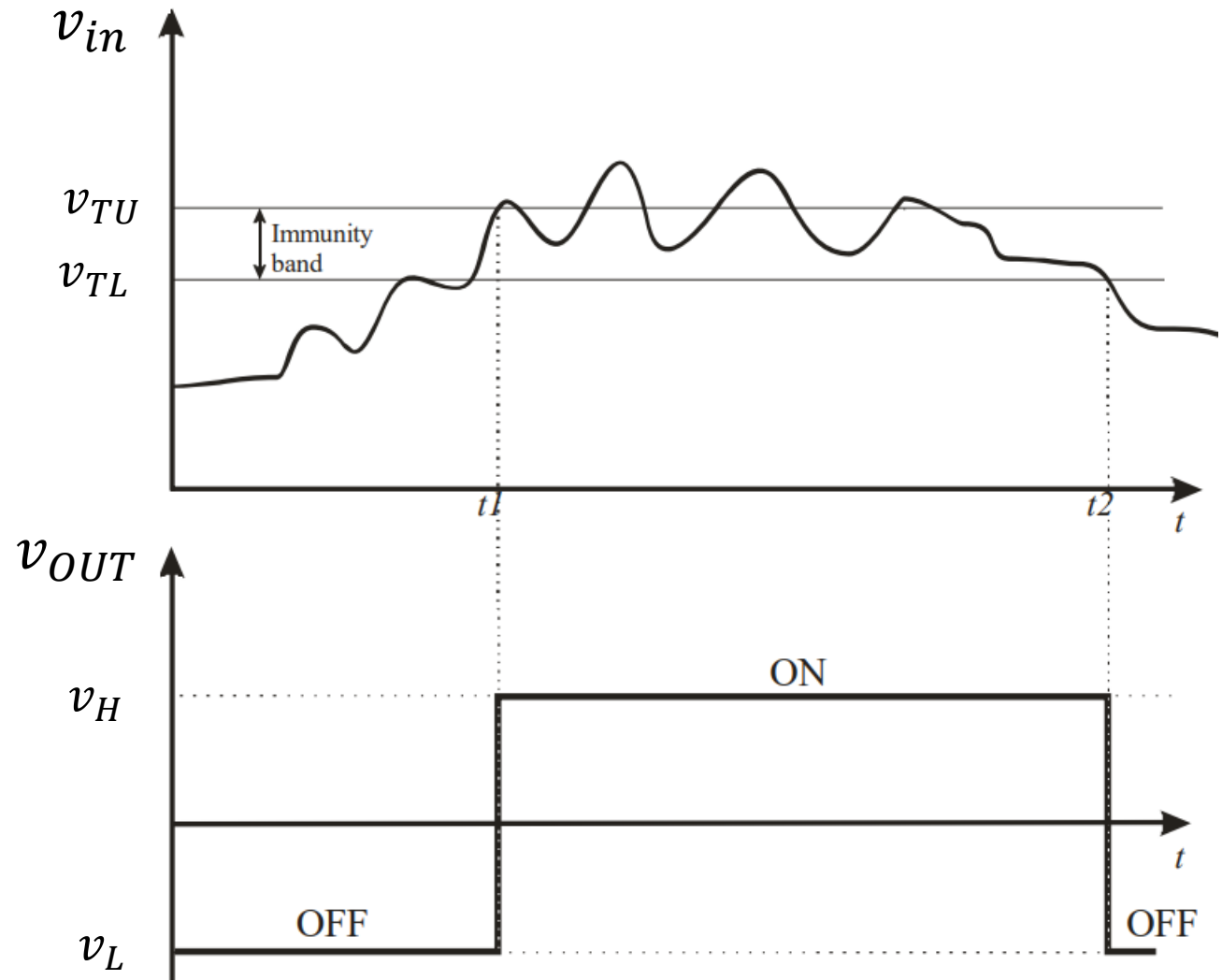- As v_{in} exceeds v_{TU} , the voltage at the output of the comparator (v_{OUT}) switches from v_L to v_H
- As v_{in} goes below v_{TL} , the voltage at the output of the comparator (v_{OUT}) switches from v_H to v_L



Positive feedback: Schmitt Trigger (Non-inverting)


- It is not negative feedback, v_+ and v_- are not always equal.

- $i_i = 0$ and $i_+ = 0$

(1) If $v_+ > v_-$, i.e., if $v_+ > 0$, $v_o = v_H$,

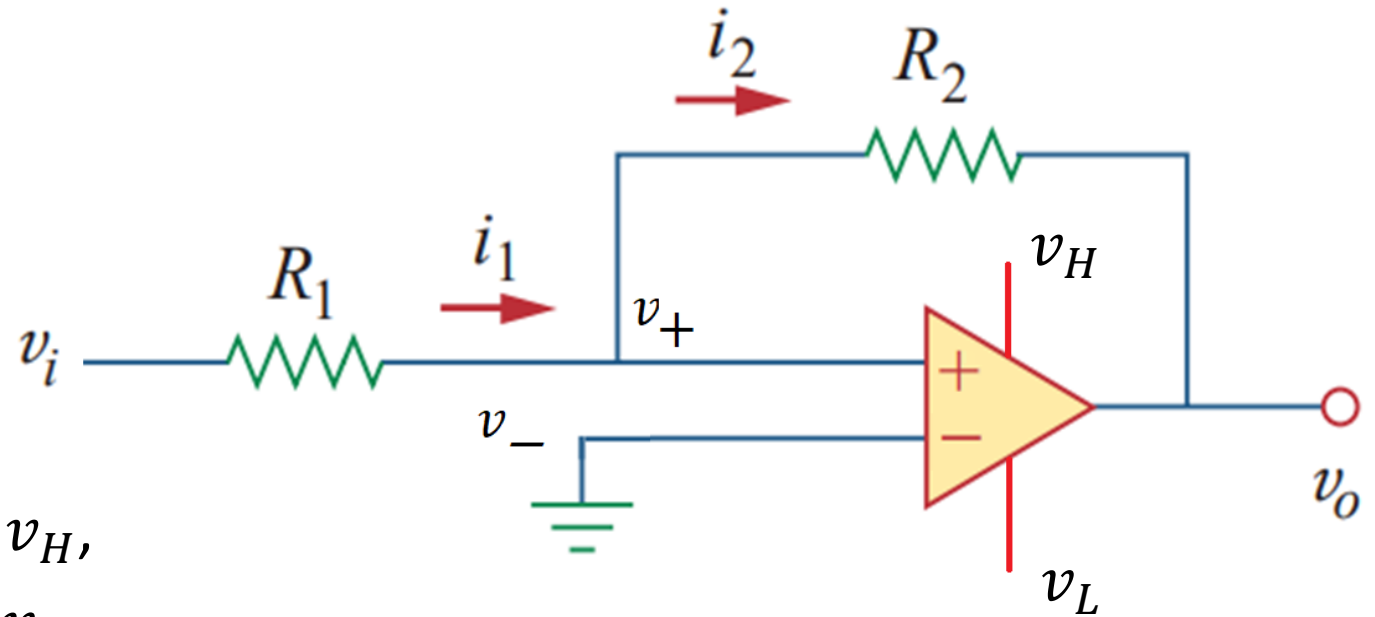(2) If $v_+ < v_-$, i.e., if $v_+ < 0$, $v_o = v_L$

- Now v_+ is connected to v_o [positive feedback], resulting in **double threshold**




Positive feedback: Schmitt Trigger (Non-inverting)

$$i_1 = \frac{v_i - v_+}{R_1} = i_2 = \frac{v_+ - v_o}{R_2}$$

$$\Rightarrow \frac{v_i}{R_1} + \frac{v_o}{R_2} = v_+ \left(\frac{1}{R_2} + \frac{1}{R_1} \right) = v_+ \left(\frac{R_1 + R_2}{R_2 R_1} \right)$$
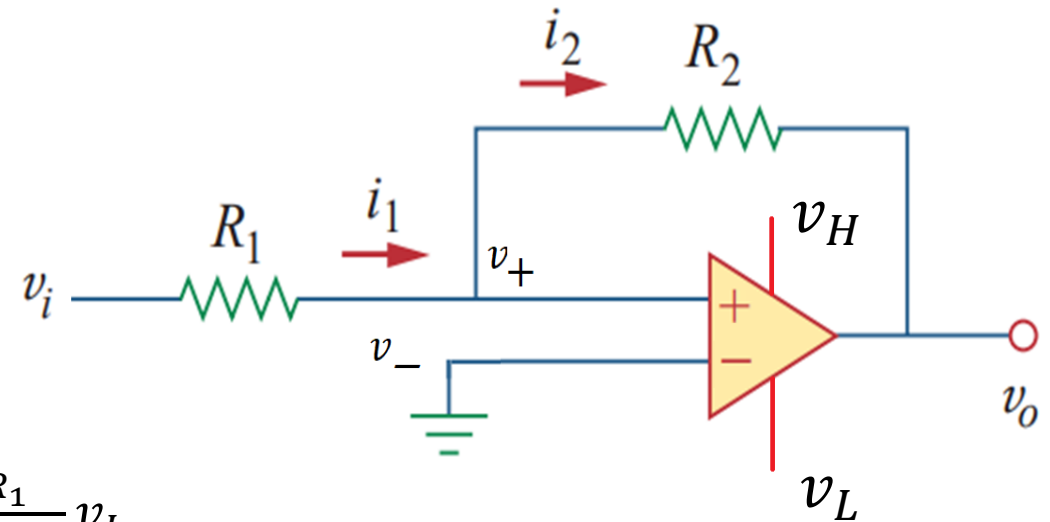
$$\Rightarrow v_+ = \frac{R_2}{R_1 + R_2} v_i + \frac{R_1}{R_1 + R_2} v_o$$



Let's consider, initially, $v_o = v_L$. So, $v_+ = \frac{R_2}{R_1 + R_2} v_i + \frac{R_1}{R_1 + R_2} v_L$

To have $v_o = v_H$, $v_+ > 0$ [see (1)], So, $\frac{R_2}{R_1 + R_2} v_i + \frac{R_1}{R_1 + R_2} v_L > 0 \Rightarrow v_i > -\frac{R_1}{R_2} v_L \leftarrow$ **Upper threshold** (v_{TU})

Let's consider, initially, $v_o = v_H$. So, $v_+ = \frac{R_2}{R_1 + R_2} v_i + \frac{R_1}{R_1 + R_2} v_H$

To have $v_o = v_L$, $v_+ < 0$ [see (2)], So, $\frac{R_2}{R_1 + R_2} v_i + \frac{R_1}{R_1 + R_2} v_H < 0 \Rightarrow v_i < -\frac{R_1}{R_2} v_H \leftarrow$ **Lower threshold** (v_{TL})

Example


If $R_1=2\text{ k}\Omega$, $R_2=2\times 2=4\text{ k}\Omega$, $v_L=-10\text{V}$, $v_H=10\text{V}$

Calculate the threshold voltages and draw the transfer characteristics.

Upper threshold, $v_{TU} = -\frac{R_1}{R_2} v_L = -\frac{2}{4}(-10) = 5\text{V}$

Lower threshold, $v_{TL} = -\frac{R_1}{R_2} v_H = -\frac{2}{4}(+10) = -5\text{V}$

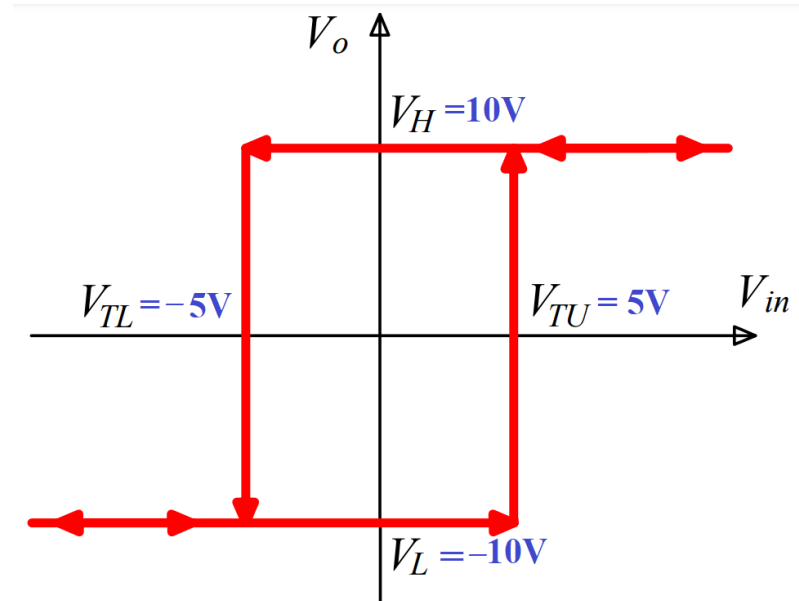
- Note that if $v_o = -10\text{V}$, it can't be $+10\text{V}$ again until v_i is above 5V (v_{TU}).
- Similarly, if $v_o = +10\text{V}$, it can't be -10V again until v_i is below -5V (v_{TL})



Schmitt Trigger with Reference Voltage

(3) If $v_+ > v_-$, i.e., if $v_+ > v_{ref}$, $v_o = v_H$,

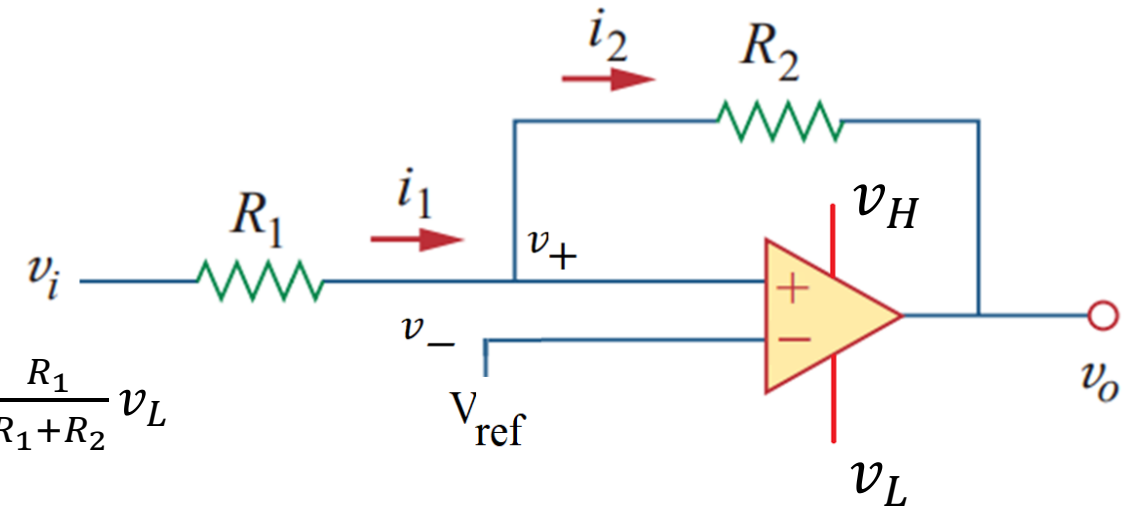(4) If $v_+ < v_-$, i.e., if $v_+ < v_{ref}$, $v_o = v_L$



Let's consider, initially, $v_+ = v_L$. So, $v_+ = \frac{R_2}{R_1+R_2} v_i + \frac{R_1}{R_1+R_2} v_L$

To have $v_o = v_H$, $v_+ > v_{ref}$ [see (3)], So, $\frac{R_2}{R_1+R_2} v_i + \frac{R_1}{R_1+R_2} v_L > v_{ref}$

$$\Rightarrow v_i > -\frac{R_1}{R_2} v_L + v_{ref} \frac{R_1+R_2}{R_2}$$

← **Upper threshold**
(v_{TU})

Let's consider, initially, $v_+ = v_H$. So, $v_+ = \frac{R_2}{R_1+R_2} v_i + \frac{R_1}{R_1+R_2} v_H$

To have $v_o = v_L$, $v_+ < v_{ref}$ [see (4)], So, $\frac{R_2}{R_1+R_2} v_i + \frac{R_1}{R_1+R_2} v_H < v_{ref}$

$$\Rightarrow v_i < -\frac{R_1}{R_2} v_H + v_{ref} \frac{R_1+R_2}{R_2}$$

← **Lower threshold**
(v_{TL})

Example


If $R_1=2\text{ k}\Omega$, $R_2=3\times 2=6\text{ k}\Omega$, $v_L=-10\text{V}$, $v_H=10\text{V}$, $v_{ref}=2.5\text{V}$

Calculate the threshold voltages and draw the transfer characteristics.

Upper threshold, $v_{TU} = -\frac{R_1}{R_2} v_L + v_{ref} \frac{R_1+R_2}{R_2} = 6.67\text{ V}$

Lower threshold, $v_{TL} = -\frac{R_1}{R_2} v_H + v_{ref} \frac{R_1+R_2}{R_2} = 0\text{ V}$

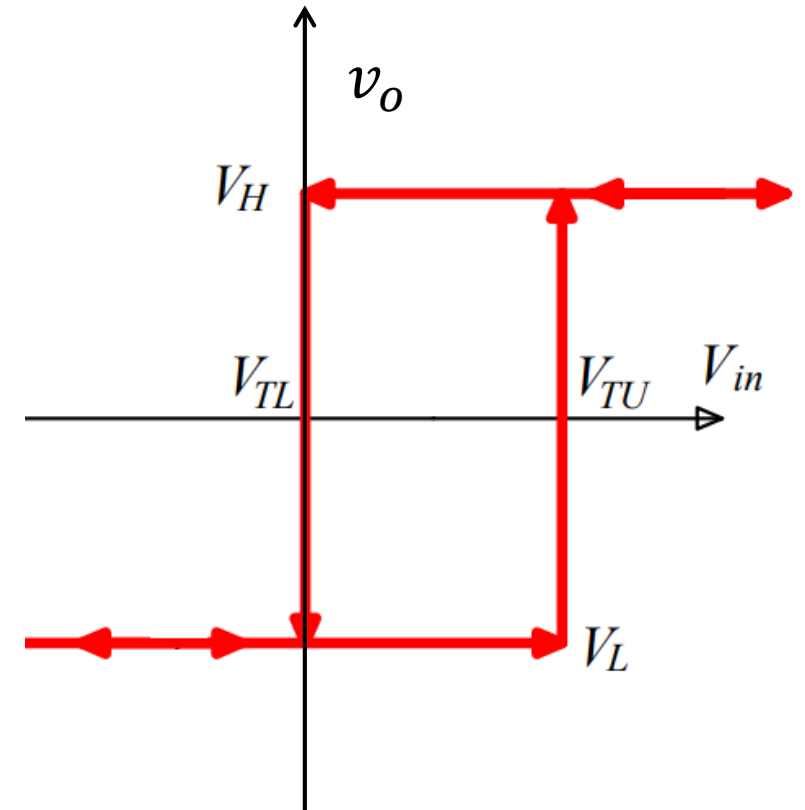- Note that if $v_o = -10\text{V}$, it can't be $+10\text{V}$ again until v_i is above 6.67V (v_{TU}).
- Similarly, if $v_o = +10\text{V}$, it can't be -10V again until v_i is below 0V (v_{TL})



How can we utilize this circuit for **water level detection**?

