

Assignment 4



BRAC University

Semester: Spring 2023

Course No: CSE251

Course Title: Electronic Devices and Circuits


Full Marks: 100

Deadline: **29 April**


2023

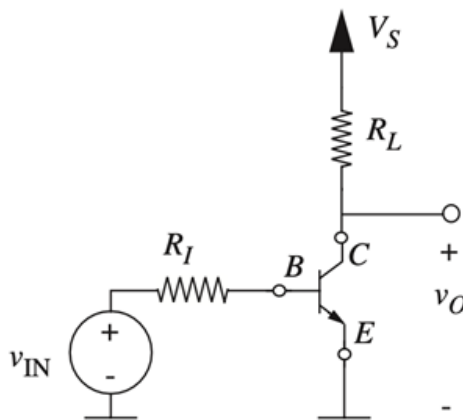1. Choose an operating point for the amplifier below to maximize the input voltage swing.

Here $R_I = 100\text{ k}\Omega$, $R_L = 10\text{ k}\Omega$, $\beta = 100$, $V_S = 10\text{ V}$



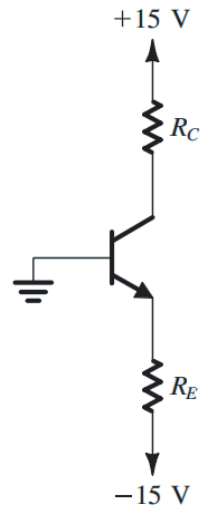2. The transistor in the circuit of Fig. shown below has $\beta = 100$ and exhibits a v_{BE} of 0.7 V at $i_C = 1\text{ mA}$. Design the circuit so that a current of 2 mA flows through the collector and a voltage of $+5\text{ V}$ appears at the collector [Use the method of assumed state to solve].



3.

In the circuit shown in Fig. the voltage at the emitter was measured and found to be -0.7 V . If $\beta = 50$, find I_E , I_B , I_C , and V_C .

