

# CSE 251 ASSIGNMENT 2


NAME: ANIKA ISLAM

ID: 21101298

SECTION: 12

# CSF 251 ASSIGNMENT 2

(1)(c)

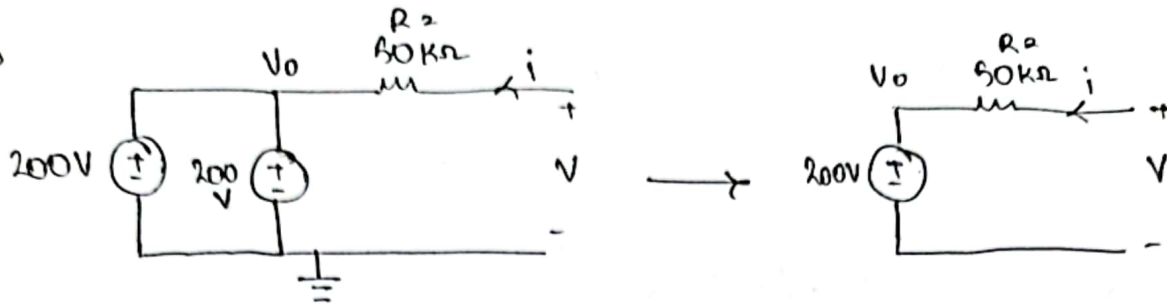

Using KCL,

$$I_1 + 200 - 200 = 0$$


$$I_1 = 0$$

$$50I + 200 - V = 0$$

$$I = \frac{V}{50} - \frac{200}{50} \left[ I = \frac{V}{R} - \frac{200}{R} \right]$$

$$I = \frac{1}{50} \cdot V - \frac{200}{50} \Rightarrow I = \left( \frac{1}{50} \right) V - 4$$

↓ ↓ ↓ ↓  
y = mx + c

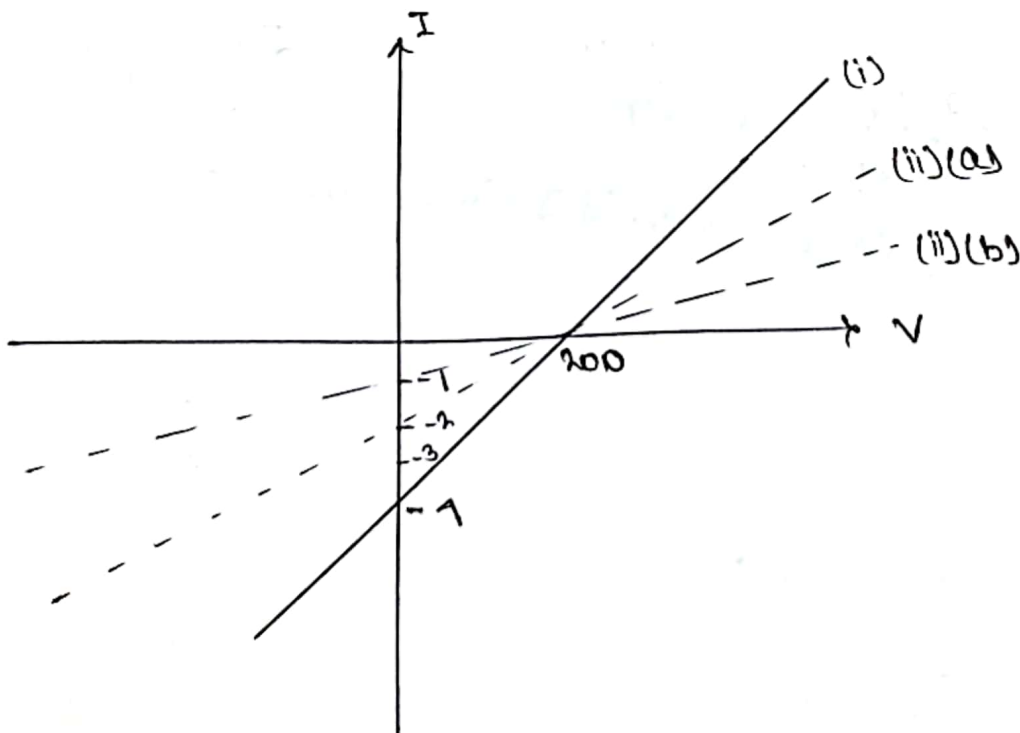

At  $I = 0$ ,

$$0 = \frac{1}{50} V - \frac{200}{50}$$

$$V = 200 \text{ V}$$

$$(ii) I = \left(\frac{V}{R}\right) - \frac{200}{R}$$

$$\text{y-intercept, } I = -\frac{200}{R}$$

$\downarrow$   
I

$$\text{x-intercept } \Rightarrow 0 = \left(\frac{1}{R}\right)V - \frac{200}{R}$$

$\downarrow$   
V

$$\Rightarrow \left(\frac{1}{R}\right)V = \frac{200}{R}$$

$$\Rightarrow V = 200$$

$\therefore$  V-intercept remains constant for any change in R.

That is <sup>V-intercept</sup> ~~R~~ is not dependent on R, whereas, I-intercept has the variable R in it, thus change in R, changes the I-intercept.

Slope =  $\frac{1}{R}$ . So, increase in R, decreases slope.

$$(a) R = 100 \text{ k}\Omega$$

$$I = \left(\frac{1}{100}\right)V - \frac{200}{100} \Rightarrow I = \left(\frac{1}{100}\right)V - 2$$

Here, R increases, so m decreases. I-intercept also changes.


$$(b) R = 200 \text{ k}\Omega$$

$$I = \left(\frac{1}{200}\right)V - \frac{200}{200} \Rightarrow I = \left(\frac{1}{200}\right)V - 1$$

Here, R increases more than that in a, so decrease in m is more. I-intercept again changes position.

(2) Part a:

(ii) For  $C_{KE} = 1$ ,

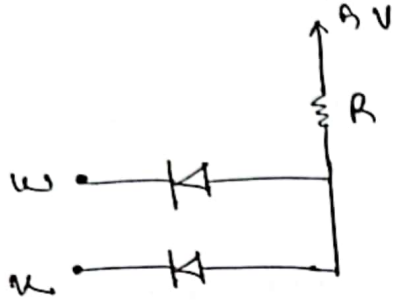


This part of the circuit gives the minimum output voltage. So, it will work like the "AND" gate.

$w$	$x$	$V_{out}$
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table for  $w$  and  $x$

$$\therefore \min(w, x) = wx$$

For ext-2.

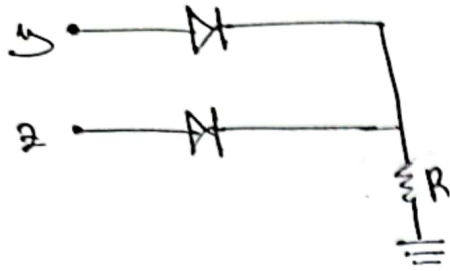

This part of the circuit gives the maximum voltage output.  
So, it will work like the "OR" gate

y	z	Vout
0	0	0
0	1	1
1	0	1
1	1	1

Truth table for y or z


$$\therefore \max(y, z) = y + z$$

(b) ckt-1 is connected to another diode. and ckt-2 is connected to a second diode, and the diodes are connected to R with 5V power supply. This gives the minimum value of f


$$f \geq (WR)(U+2)$$

part b

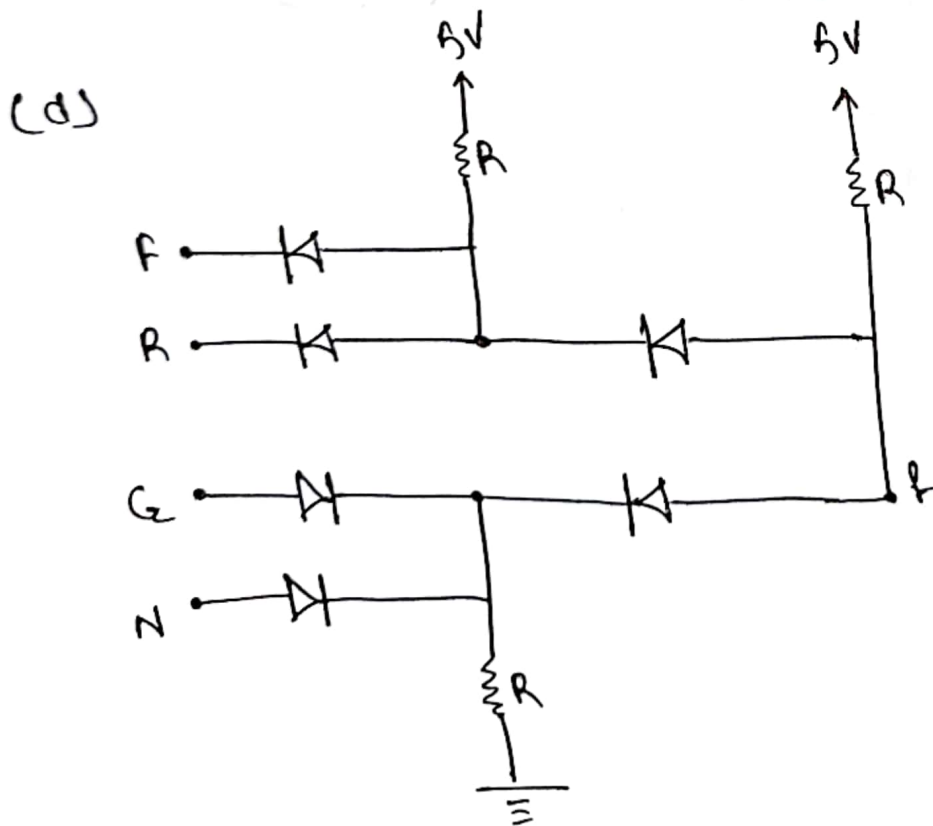(c) For the request to be considered, condition 1 and 2 need to be fulfilled at first. So, F AND R. Then condition 3 ~~or~~ 4 need to be fulfilled, so G ~~or~~ N. Finally, condition 1 and condition together with condition 3 or 4 must be satisfied. Thus,  $(FR)(G+N) \geq f$



(3) (i) let  $D1 - ON, D2 - ON$

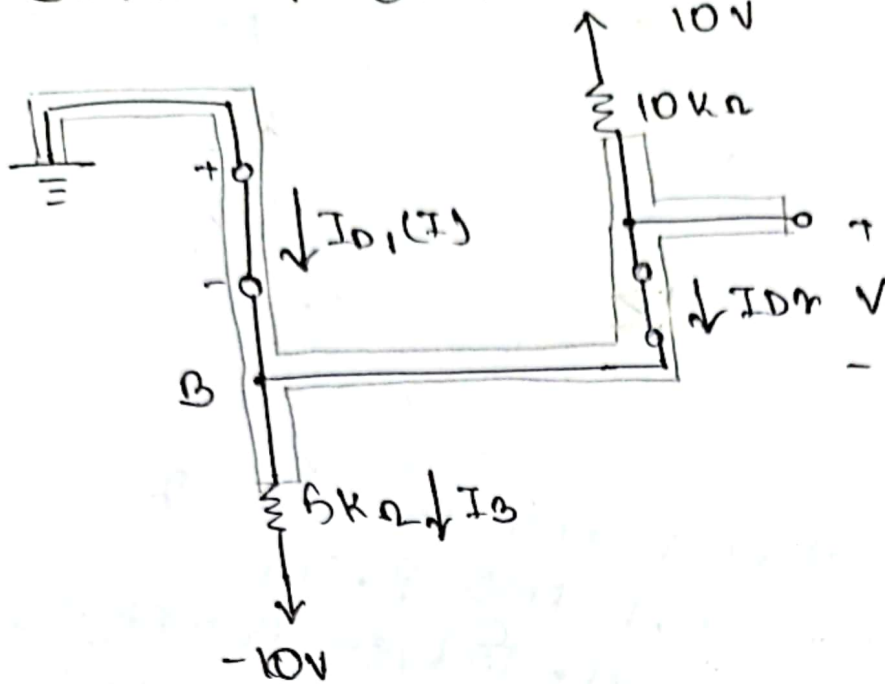

$$I_{D2} = \frac{10 - 0}{10} \Rightarrow I_{D2} = 1 \text{ mA} \text{ } \checkmark$$

$$I_{D1} + I_{D2} = I_B$$


$$I_{D1} = \frac{0 - (-10)}{10} = 1 \Rightarrow I_{D1} = 1 \text{ mA} \text{ } \checkmark$$

$\therefore$  The assumption is correct.

$$I = I_{D1} = 1 \text{ mA}$$

$$V = 10 \text{ V}$$

(ii) Let  $D1 - ON, D2 - ON$

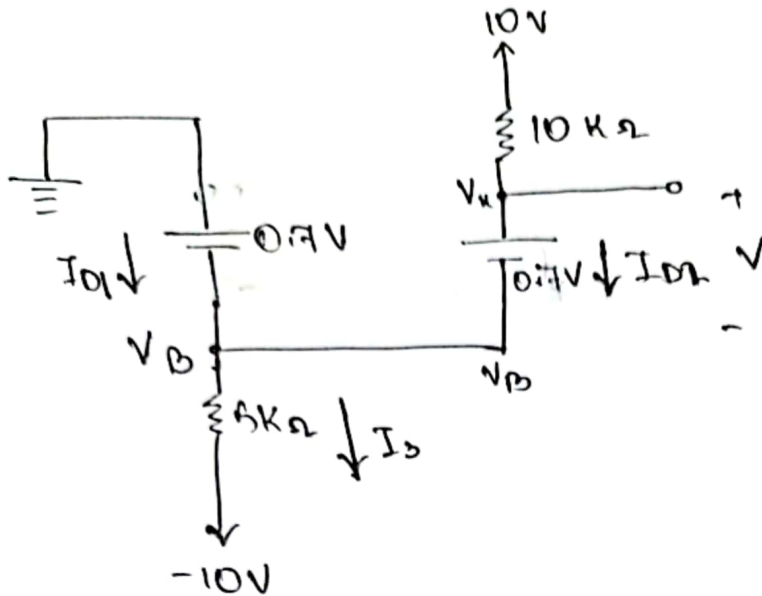

$$0 - V_B = 0.7$$

$$V_B = -0.7V$$

$$V_u = V_B = -0.7$$

$$V_u - (-0.7) = 0.7$$

$$V_u = 0V$$

$$I_{D2} = \frac{10 - V_u}{10} \Rightarrow \frac{10 - 0}{10} \Rightarrow I_{D2} = 1mA \approx 10mA \checkmark$$

$$I_{D1} + I_{D2} = I_3$$

$$I_{D1} = \left( \frac{-0.7 - (-10)}{5} \right) = 1 \Rightarrow I_{D1} = 0.86mA \approx 0mA \checkmark$$


∴ The assumption is correct.

$$I_3 = I = 0.86mA$$

$$V = V_u = 0V$$



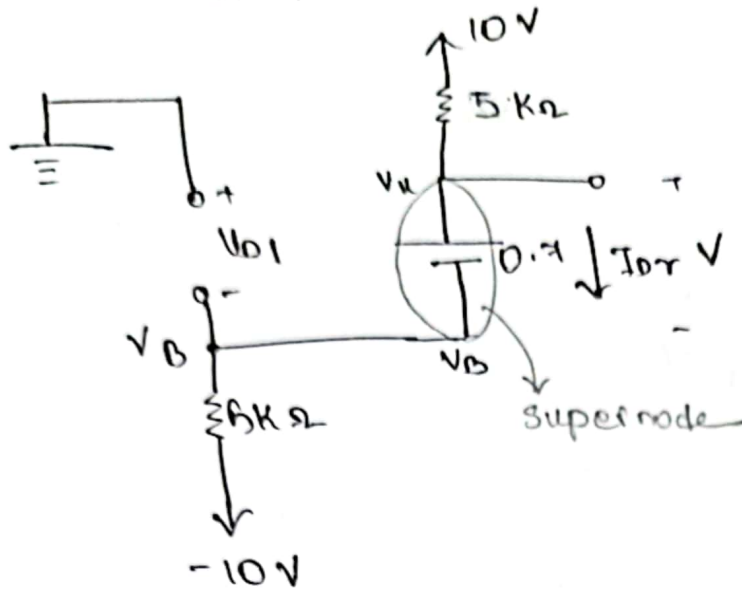(iii) Let  $D1 - \text{OFF}, D2 - \text{ON}$



$$V_A - V_B = 0.7 \Rightarrow V_A = V_B + 0.7$$

$$\frac{V_B - (-10)}{5} + \frac{V_A - 10}{5} = 0$$

$$\frac{V_B + 10}{5} + \frac{(V_B + 0.7) - 10}{5} = 0$$

$$V_B = -0.35 \text{ V}$$

$$I_{D2} = \frac{10 - (-0.35 + 0.7)}{5} \Rightarrow I_{D2} = 1.93 \text{ mA} > 0 \text{ mA} \checkmark$$

$$V_{O1} = 10 - (-0.35) \Rightarrow V_{O1} = 0.35 \text{ V} < 0.7 \text{ V} \checkmark$$


The assumption is correct

$$I_{D1} = I = 0 \text{ mA}$$

$$V = V_A = -0.35 + 0.7 = 0.35 \text{ V}$$

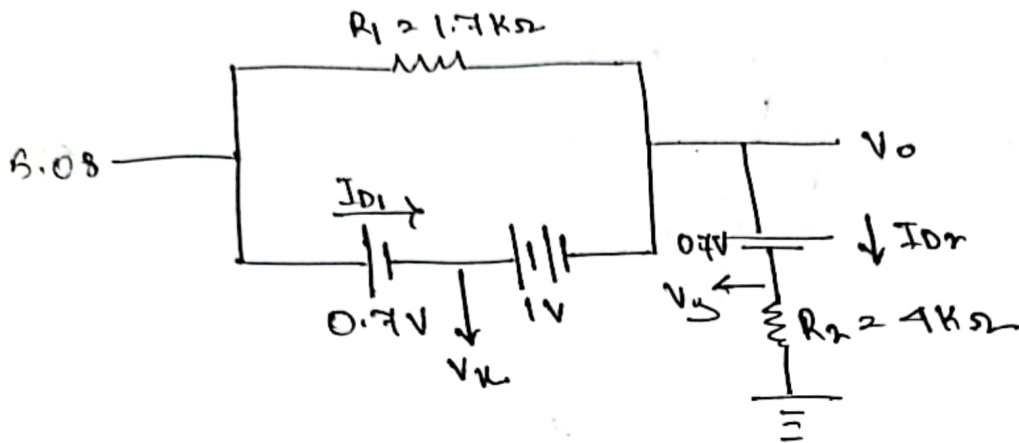(4) Assumption:  $D1 - ON, D2 - ON$

$$V_I = 5 + 8 \times 10^{-2} = 5.08 \text{ V}$$



$$5.08 - V_K = 0.7 \Rightarrow V_K = 4.38 \text{ V}$$

$$V_K - V_0 = 1 \Rightarrow V_0 = 3.38 \text{ V}$$


$$V_0 - V_Y = 0.7 \Rightarrow V_Y = 4.08 \text{ V}$$

$$I_{D1} = \frac{V_0 - 5.08}{1.7} \Rightarrow I_{D1} = \frac{3.38 - 5.08}{1.7} \Rightarrow I_{D1} = -1.0 \text{ mA} \neq 0 \text{ mA}$$

$$I_{Dr} = \frac{V_Y - 0}{4} \Rightarrow I_{Dr} = \frac{4.08 - 0}{4} \Rightarrow I_{Dr} = 1.02 \text{ mA} \neq 0 \text{ mA}$$

The assumption is wrong.

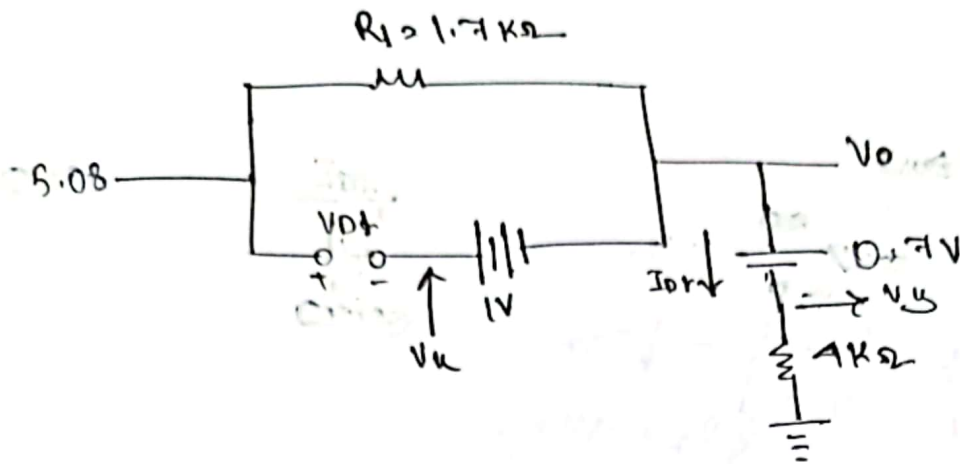modified assumption:  $D1 - \text{OFF}, D2 - \text{ON}$



$$1.7I + V_{D1} + 1 = 0$$

$$1.7I + (5.08 - V_{01}) + 1 = 0$$

$$1.7I + (5.08 - (1 + V_0)) + 1 = 0$$

$$1.7I + 5.08 - 1 - V_0 + 1 = 0$$

$$1.7(0) + 5.08 - V_0 = 0$$

$$V_0 = 5.08 \text{ V}$$

$$5.08 - V_u = V_{01}$$

$$V_u - V_0 = 1 \Rightarrow V_u = 1 + V_0$$

$$V_0 - V_u = 0.7 \Rightarrow 5.08 - V_u = 0.7 \Rightarrow V_u = 4.38 \text{ V}$$

$$V_u = 1 + 5.08 = 6.08 \text{ V}$$

$$V_{D1} = 5.08 - V_u = 5.08 - 6.08 = -1 \text{ V} < 0.7 \text{ V} \checkmark$$

$$I_{02} = \frac{V_u - 0}{4} = \frac{4.38 - 0}{4} = 1.095 \text{ mA} > 0 \text{ mA}$$

$\therefore$  The assumption is correct.

$$I_{R1} = \frac{5.08 - V_0}{1.7} = \frac{5.08 - 5.08}{1.7} = 0 \text{ mA}$$

$$I_{D1} = 0 \text{ mA}$$

$$I_{D2} = 1.095 \text{ mA}$$

$$V_0 = 5.08 \text{ V}$$