

# Lecture 3

Introduction to OpAmp

# Review



- Last class: alternative representation, KCL, KVL, nodal
- Today: **review** of dependent source, introduction to amplifiers, operational amplifiers

# Dependent Source

- Active sources – either voltage or current source
- Difference: voltage (or current) controlled by the voltage/current in a different branch
- Technically non-linear devices – because in real life, dependent sources are made using non-linear electronic devices (e.g. MOSFET)
- However, analysis are similar to linear circuits (CSE250), hence we will start with this


# Major Difference

Independent devices:

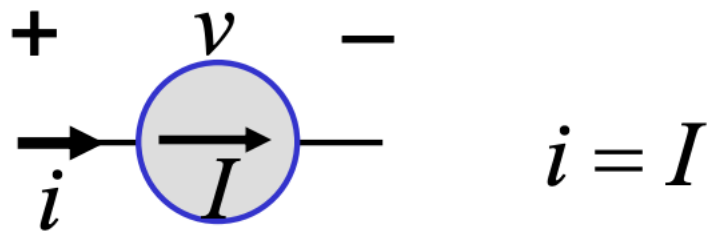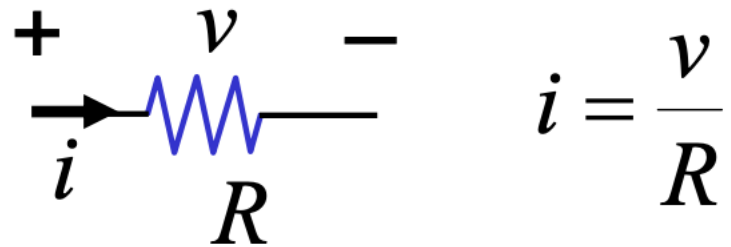


2 terminals, 1 port

Dependent devices:

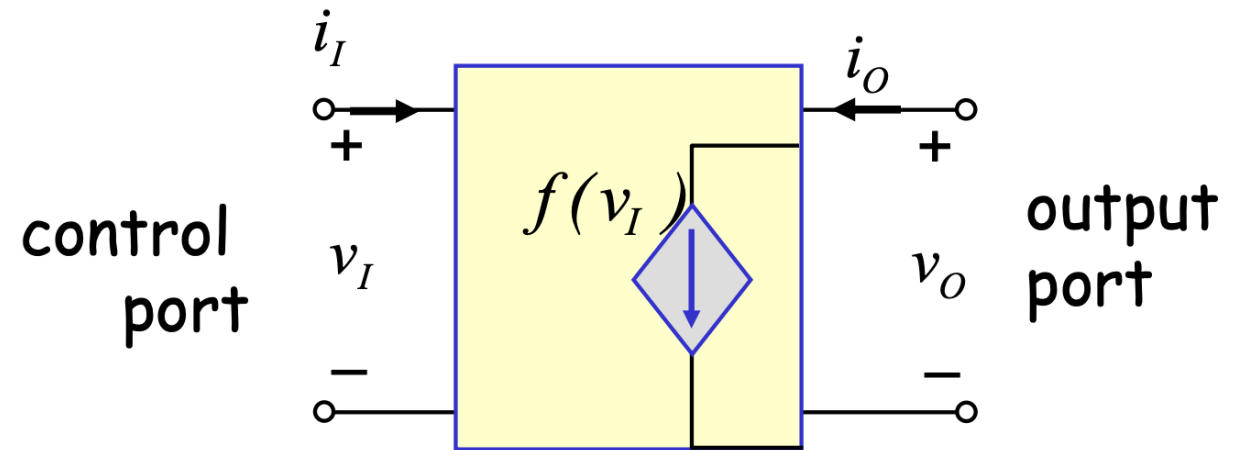

2 terminals, 2 port


# Example 1

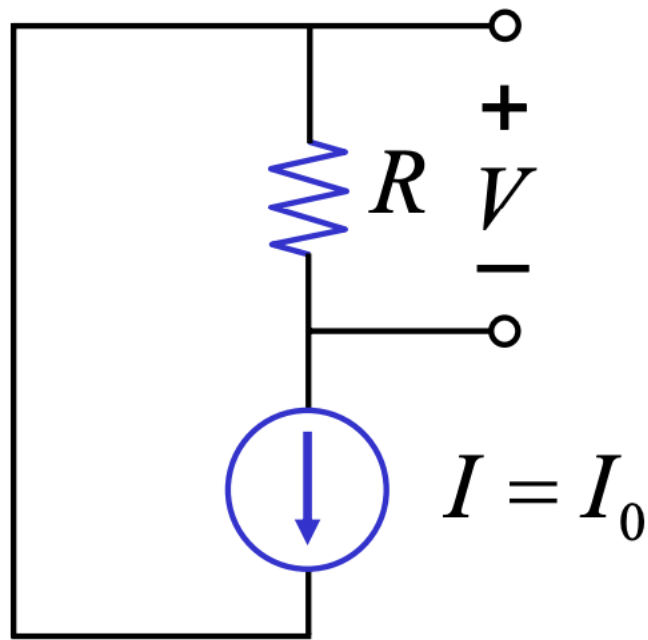


Find  $V$

(Ans:  $V = I_0 R$ )

## Example 2

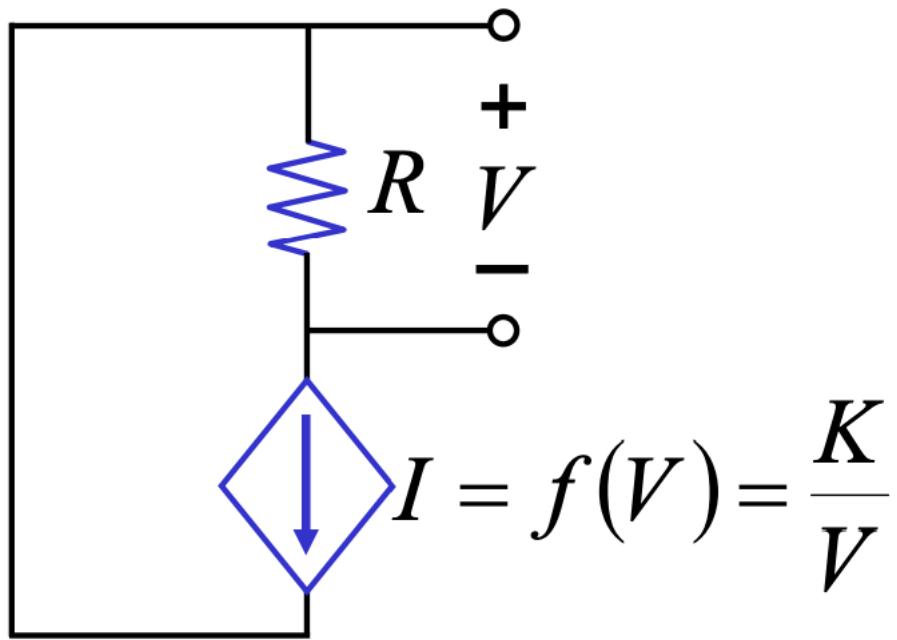

Find  $V$


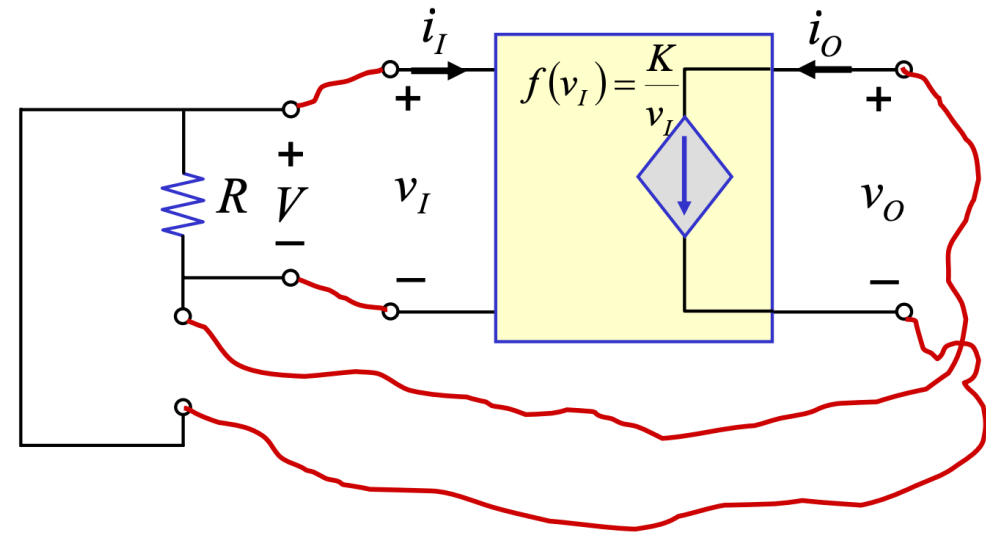


$$\begin{aligned} \text{Ans: } V &= IR \Rightarrow V = \left(\frac{K}{V}\right) R \\ &\Rightarrow V^2 = KR \Rightarrow V = \sqrt{KR} \end{aligned}$$

Application of dependent sources: amplifiers!

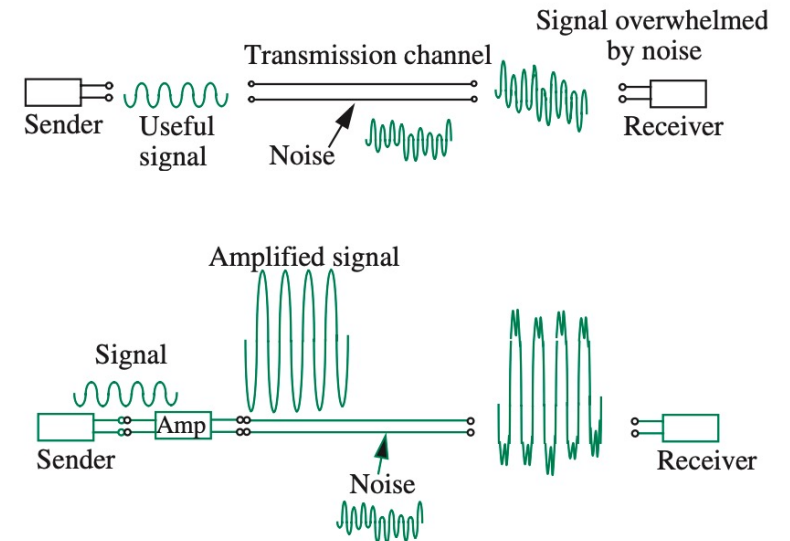
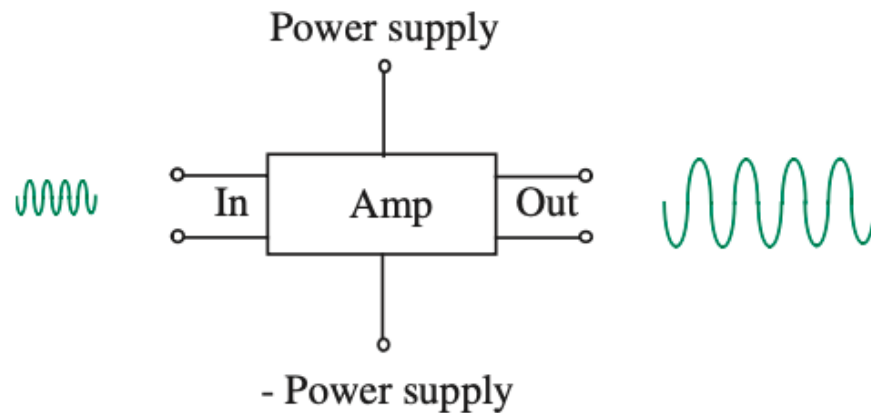
# Amplifier

- Linear amplifier  $\Rightarrow OUT = k \times IN$ .  $k$  is called the **gain** of the amplifier
- OUT/IN can be voltage or current
- Amplifier must provide power gain ( $P_{OUT} > P_{IN}$ ), hence need **power supply**
- Usage: communication


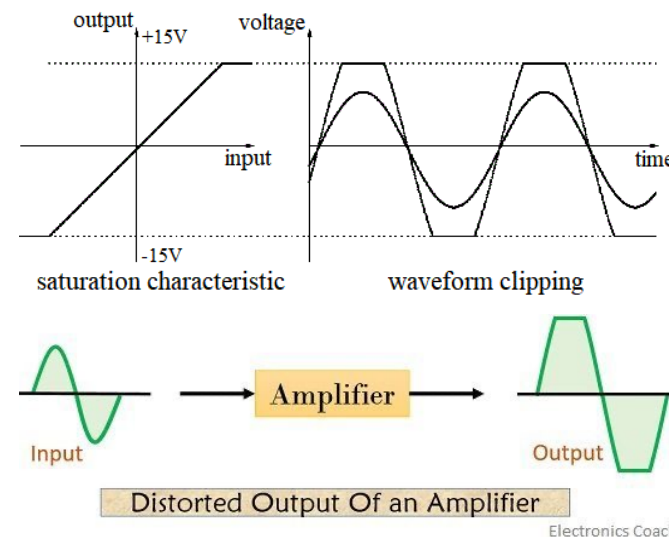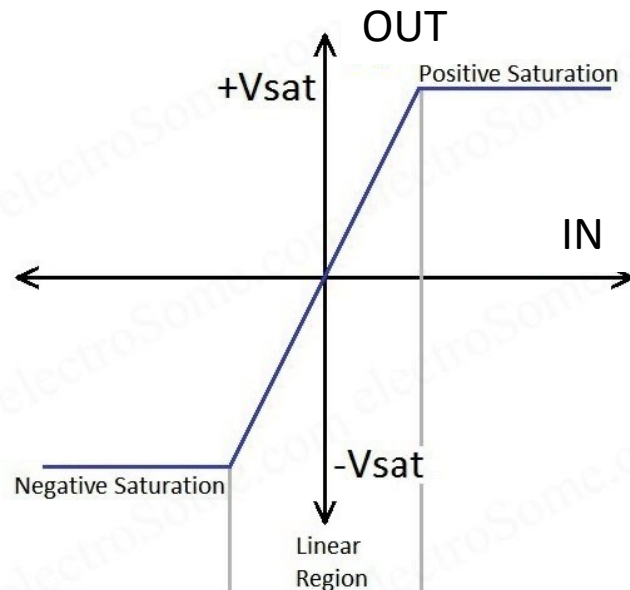
# Transfer Characteristics of Amplifiers

- $y = mx$ , hence straight line going through origin. Here,  $m = k = \text{gain}$
- Saturation due to limited power supply. Output cannot be greater than P.S.
- Input must be within a **valid input range**, otherwise output will be distorted
- Amplifiers are **non-linear devices**, because they are made using dependent sources








# Operational Amplifiers

- An operational amplifier, or **op-amp** for short, is a versatile and powerful integrated circuit that is widely used in a variety of electronic applications.
- An Op-Amp is designed so that it performs some mathematical operations when external components, such as resistors and capacitors, are connected to its terminals.
- The op amp is an electronic device consisting of a complex arrangement of resistors, transistors, capacitors, and diodes. A full discussion of what is inside the op amp is beyond the scope of this course. For now, it will suffice to treat the op amp as a circuit building block and simply study what takes place at its terminals.

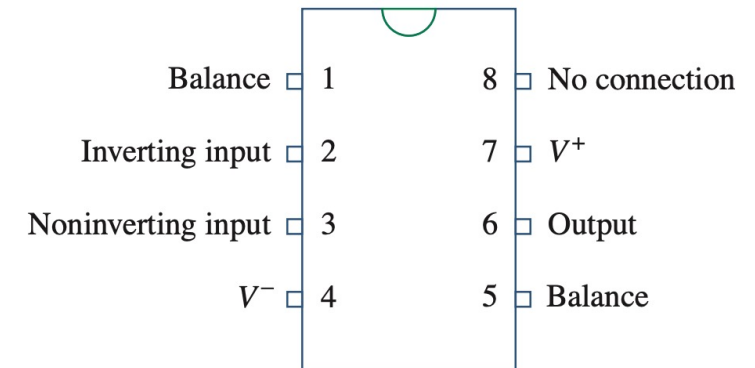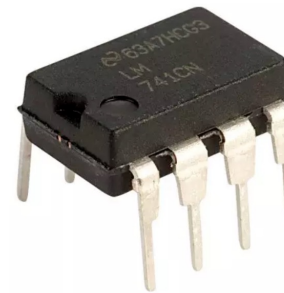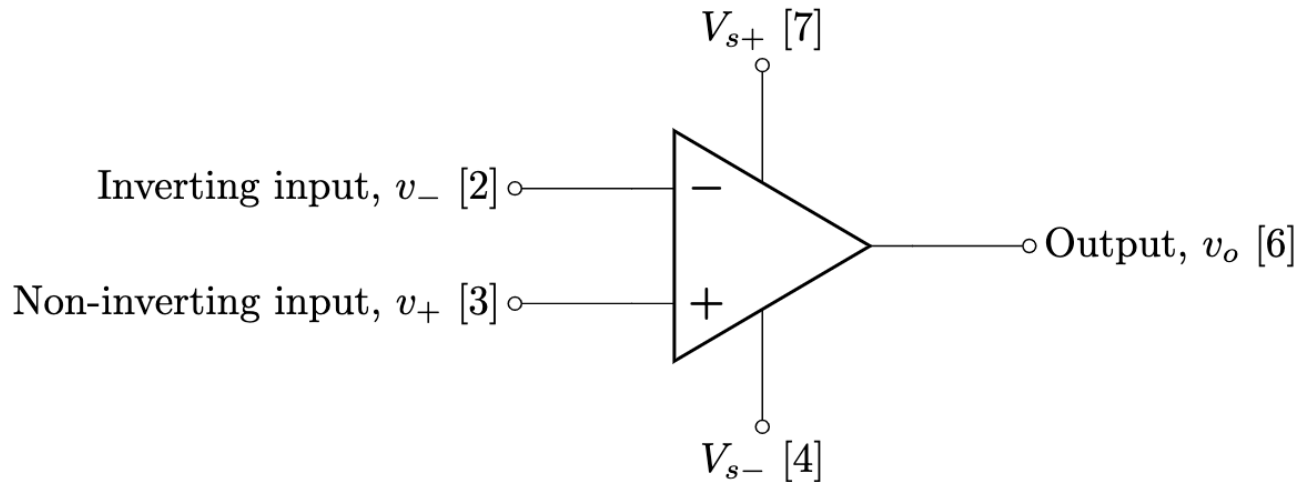
# Terminals and Circuit Symbol

- Op-amps are **differential amplifiers** – meaning it amplifies the voltage difference between two terminals. Therefore, it has two inputs
- Since this is an amplifier, there are two terminals for **power supply**


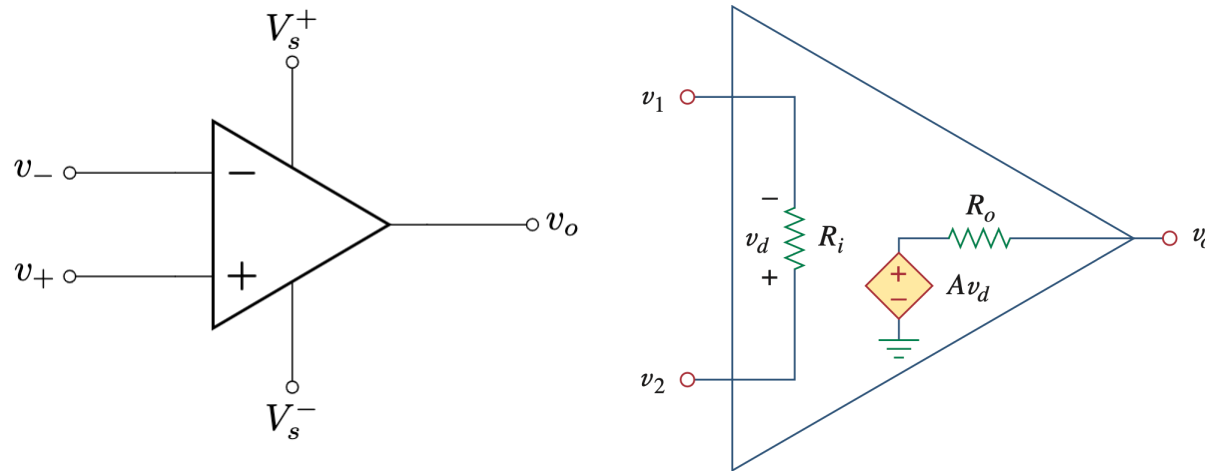
# Equivalent Circuit

Since op amp is an amplifier, the internal circuit can be modeled using a **voltage controlled voltage source** (VCVS)! (actual circuit is complicated)



$v_1 = v_-$  = voltage of inverting terminal  
 $v_2 = v_+$  = voltage of noninverting terminal

$v_d = v_+ - v_- = v_2 - v_1$   
= differential input voltage for VCVS

$A$  = Open loop gain

$R_i$  = Input resistance


$R_o$  = Output resistance

The op amp senses the difference between the two inputs, multiplies it by the gain  $A$ , and causes the resulting voltage to appear at the output. Thus, the output  $v_o$  is given by

$$v_o = Av_d = A(v_2 - v_1) = A(v_+ - v_-)$$
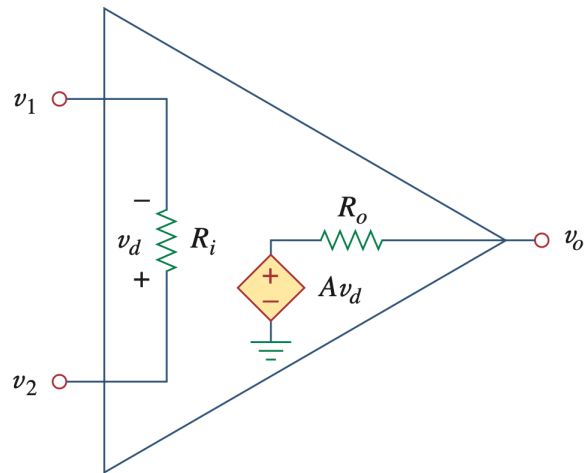
# Equivalent Circuit

Since op amp is an amplifier, the internal circuit can be modeled using a **voltage controlled voltage source** (VCVS)! (actual circuit is complicated)



$v_1 = v_-$  = voltage of inverting terminal

$v_2 = v_+$  = voltage of noninverting terminal

$v_d = v_+ - v_- = v_2 - v_1$   
= differential input voltage for VCVS

$A$  = Open loop gain

$R_i$  = Input resistance

$R_o$  = Output resistance

Parameter	Typical Range
$A$	$10^4 - 10^8$
$R_i$	$100\text{ k}\Omega - 10^{10}\text{ k}\Omega$
$R_o$	$0.01\text{ k}\Omega - 0.1\text{ k}\Omega$


The op amp senses the difference between the two inputs, multiplies it by the gain  $A$ , and causes the resulting voltage to appear at the output. Thus, the output  $v_o$  is given by

$$v_o = Av_d = A(v_2 - v_1) = A(v_+ - v_-)$$

# Practical Limitation - Saturation


- Similar to amplifiers, the output of op-amp is limited by power supply (Saturation)
- Op-amp can operate in three modes, depending on  $v_d$ :
  - Positive saturation:  $v_o = V_s^+ = V_{CC}$
  - Linear region:  $-V_{CC} < v_o = Av_d < V_{CC}$  [Slope =  $A$ ]
  - Negative saturation:  $v_o = V_s^- = -V_{CC}$
- If we attempt to increase  $v_d$  beyond the linear range, the op-amp becomes saturated and yields  $v_o = V_{CC}$  or  $v_o = -V_{CC}$ . That is the output voltage is restricted by

$$-V_{CC} \leq v_o \leq V_{CC}$$

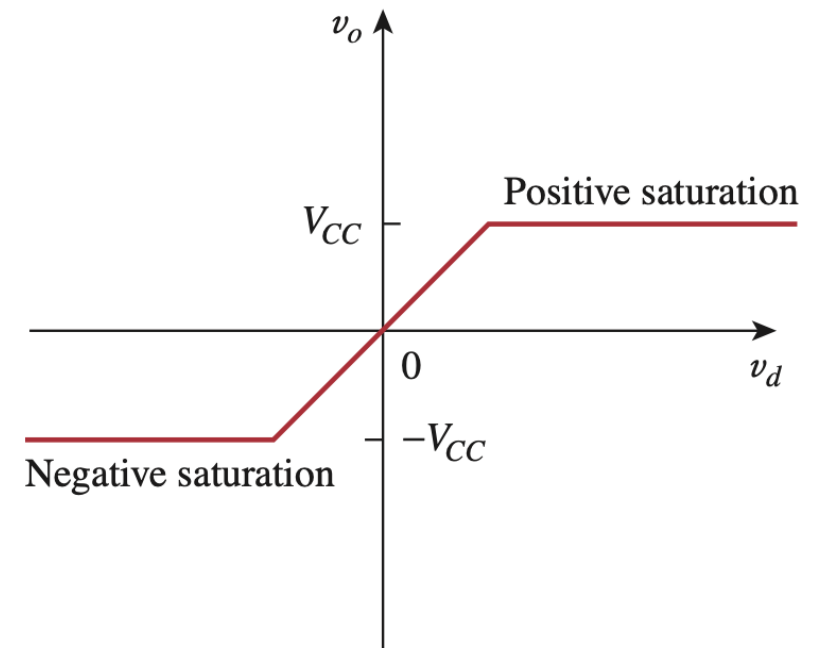

# Example 3

- Find  $v_o$

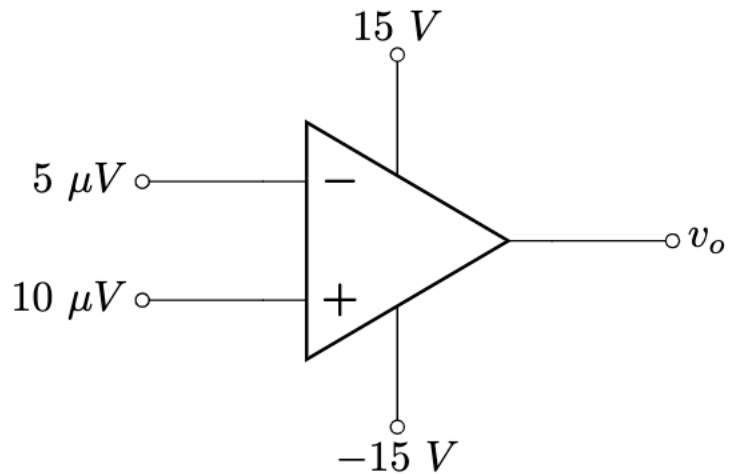

$$A = 2 \times 10^5$$


**Solution:**

$$v_d = v_+ - v_- = 10\ \mu V - 5\ \mu V = 5\ \mu V$$
$$\Rightarrow v_o = Av_d = (2 \times 10^5) \times (5 \times 10^{-6}) = 1\ V$$

Since this is in between  $-V_{CC}$  and  $V_{CC}$ , output valid

# Example 4

- Find  $v_o$

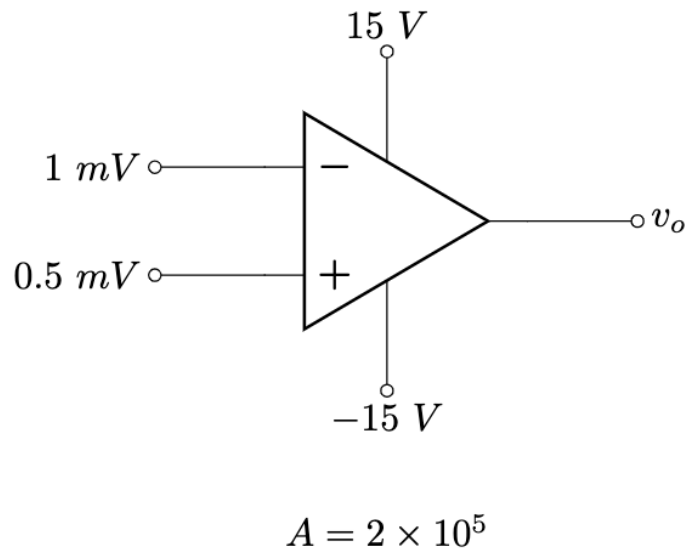

## Solution:

$$v_d = v_+ - v_- = 1 \text{ mV} - 0.5 \text{ mV} = 0.5 \text{ mV}$$
$$\Rightarrow v_o = Av_d = (2 \times 10^5) \times (0.5 \times 10^{-3}) = 100 \text{ V}$$

However, the output must be limited between  $-V_{CC}$  and  $V_{CC}$ . Therefore, the highest output voltage can be  $V_{CC} = 15 \text{ V}$ .

$$\therefore v_o = 15 \text{ V}$$

# Solving Circuit with Op-Amp

- Don't be scared! Circuit solving with op-amp is exactly same as the circuits you solved in CSE250
- Step 1: replace with equivalent circuit
- Step 2: solve using KCL & KVL, or nodal analysis (linear)
- In most cases, the power supply voltages are not mentioned. **Hence, we will assume the output is within the linear range in this case**





# Example 5

Find  $i_F$  and  $v_o$ . Here,  $R_i = 200\text{ k}\Omega$ ,  $R_o = 0.1\text{ k}\Omega$ ,  $A = 2 \times 10^5$


**Solution:**

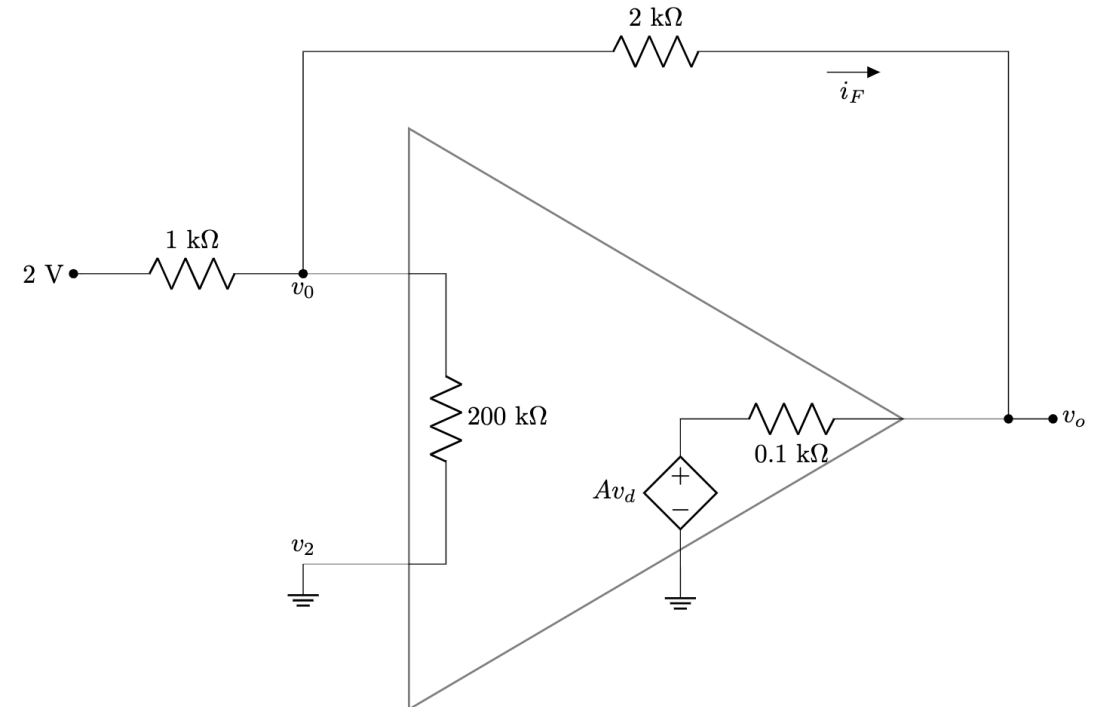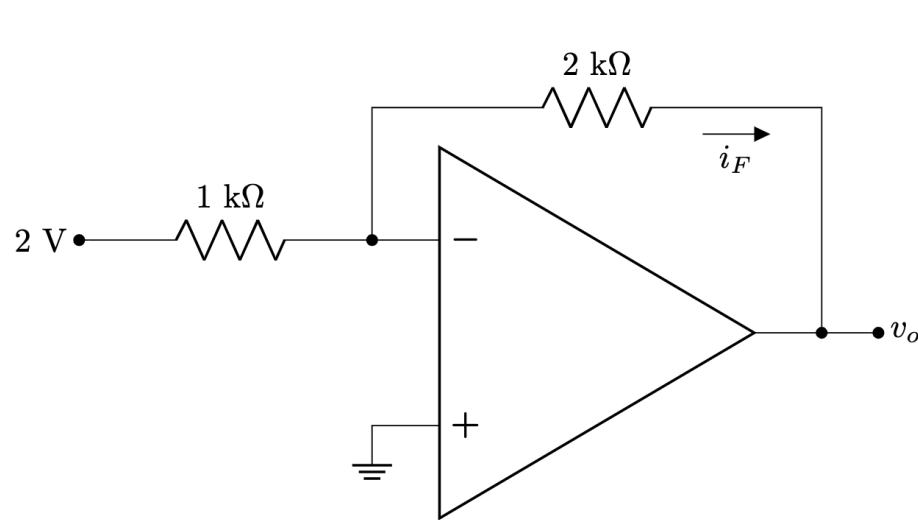**Step 1: replace using equivalent circuit**




# Example 5

Step 2: Solve using KCL & KVL or nodal

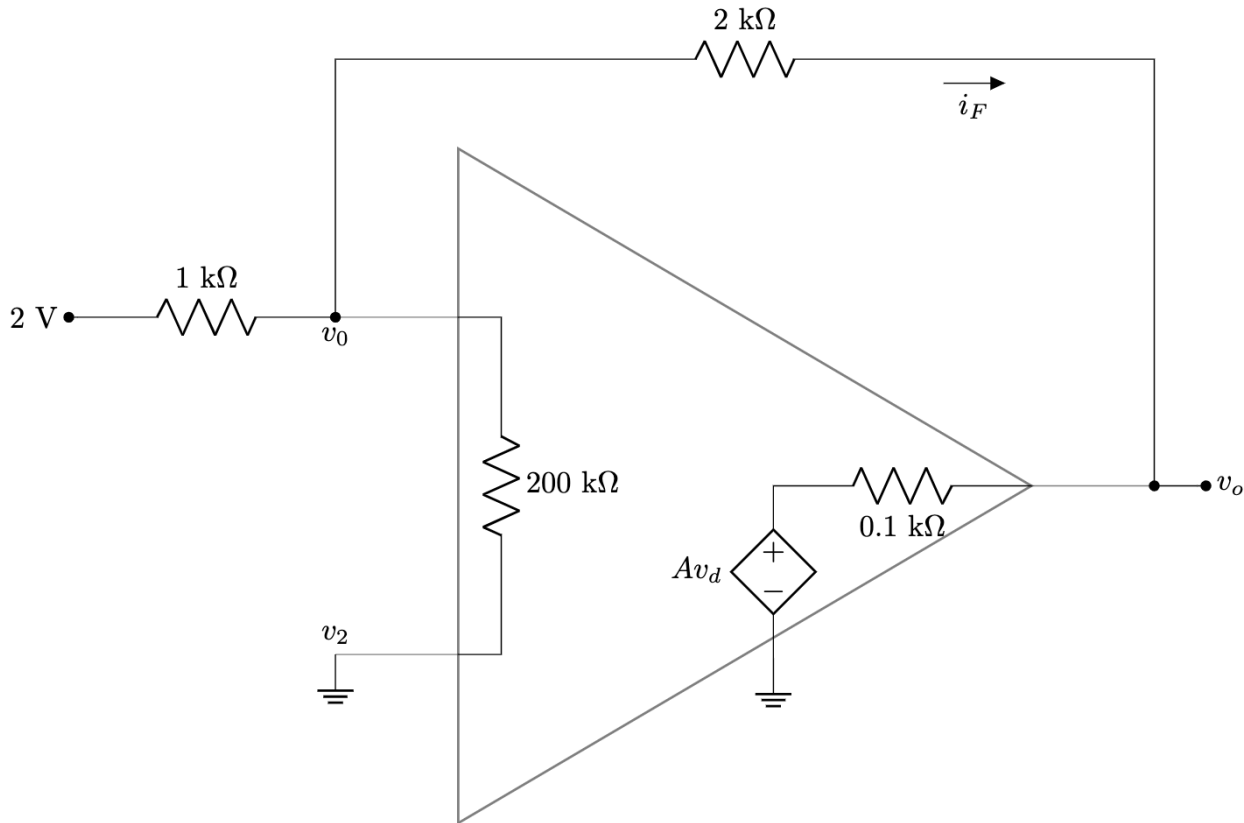


# Example 5

Step 2: Solve using KCL & KVL or nodal

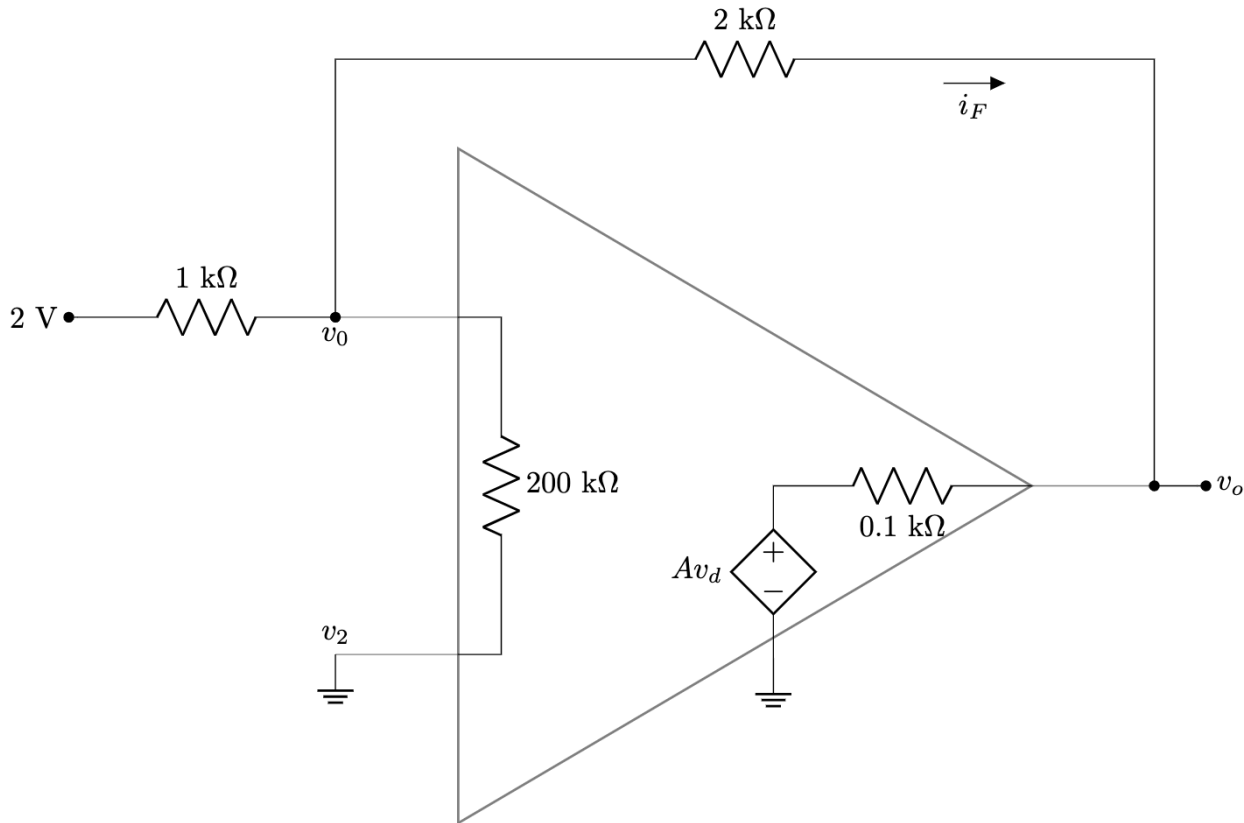
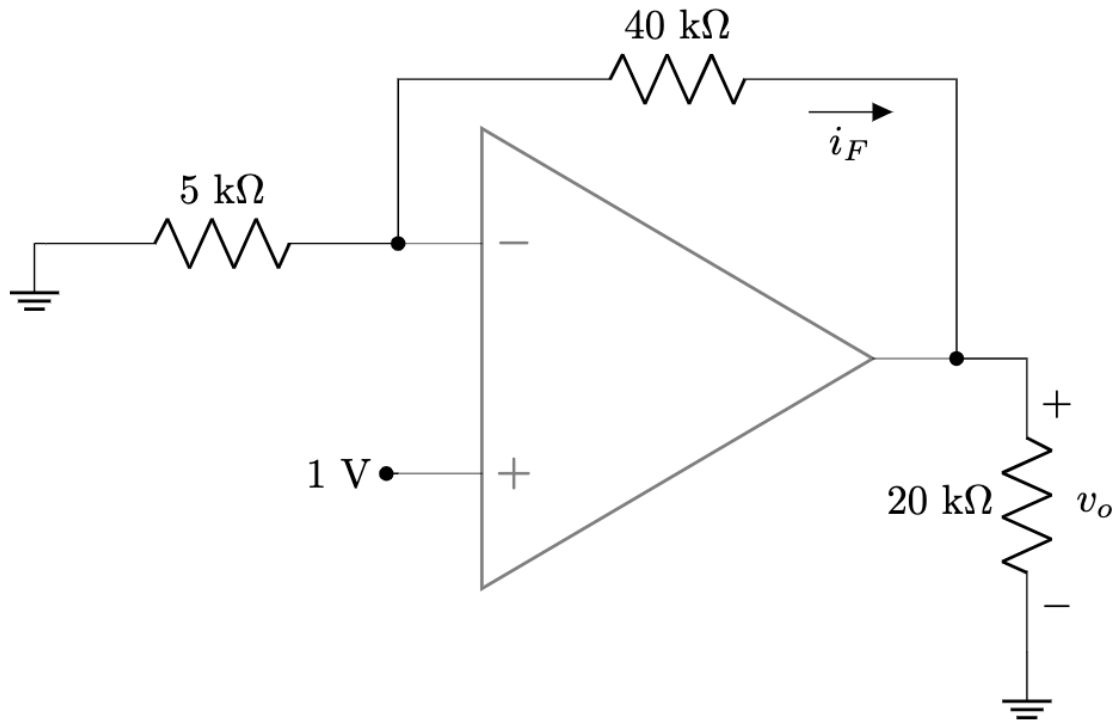
# Example 6

Find  $i_F$  and  $v_o$ . Here,  $R_i = 200\text{ k}\Omega$ ,  $R_o = 0.1\text{ k}\Omega$ ,  $A = 2 \times 10^5$




# The Ideal Op-Amp

- To facilitate the understanding of op amp circuits, we will assume **ideal op amps**
  - Infinite open-loop gain,  $A = \infty$
  - Infinite input resistance,  $R_i = \infty = \text{open circuit}$
  - Zero output resistance,  $R_o = 0 = \text{short circuit}$
- Although an ideal op amp provides only an approximate analysis, most modern amplifiers have such large gains and input impedances that the approximate analysis is a good one.
- **Circuit solving become much simpler.** As  $R_i = \infty$ ,  $i_1 = i_2 = 0$
- Since  $A = \infty$ , in open-loop configuration,  $v_o$  will either be positive saturated or negative saturated (why?)

$$v_o = \begin{cases} V_s^+ & \text{if } v_d > 0 \Rightarrow v_2 > v_1 \\ V_s^- & \text{if } v_d < 0 \Rightarrow v_2 < v_1 \end{cases}$$

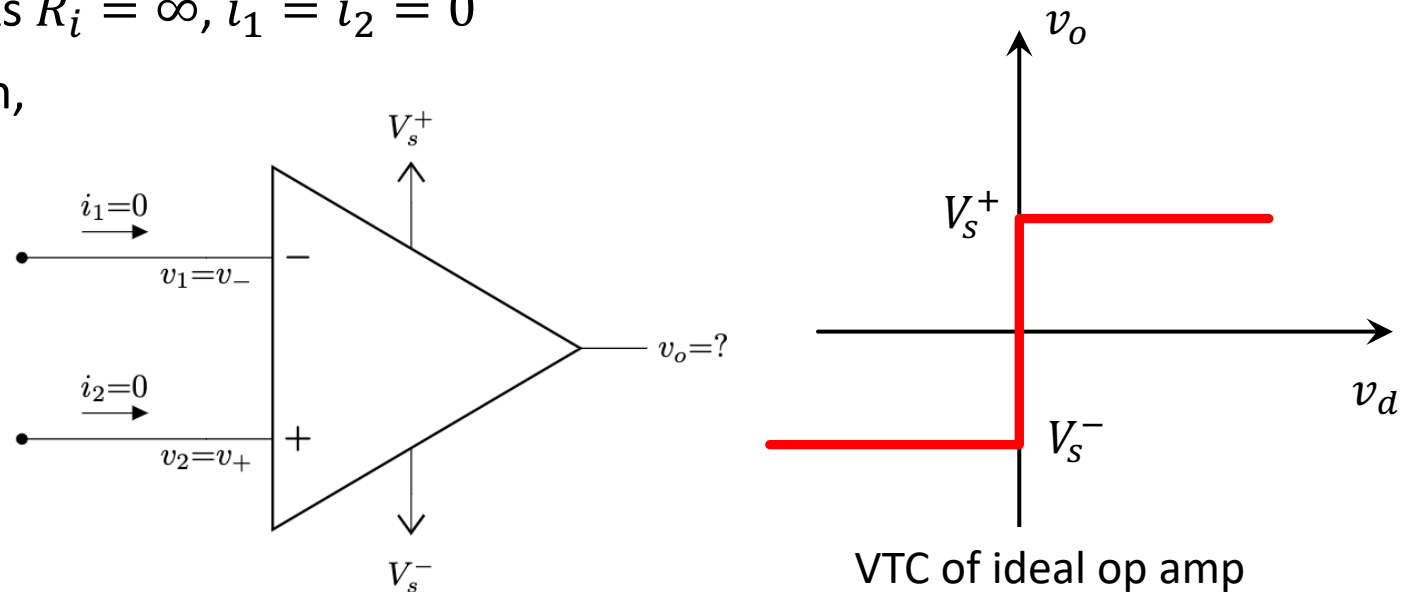**Reminder:**  $v_d = v_2 - v_1 = v_+ - v_-$



# Application - Comparator

- A comparator compares two voltages to determine which is larger.
- The comparator is essentially an op-amp operated in an open-loop configuration
- Two types –
  - (1) **Non-inverting**: outputs a positive voltage ( $V_H = V_S^+$ ) when input is greater than reference
  - (2) **Inverting**: outputs a negative voltage ( $V_L = V_S^-$ ) when input is greater than reference
- Application – smoke detector, turning AC on/off automatically, etc (next lecture)

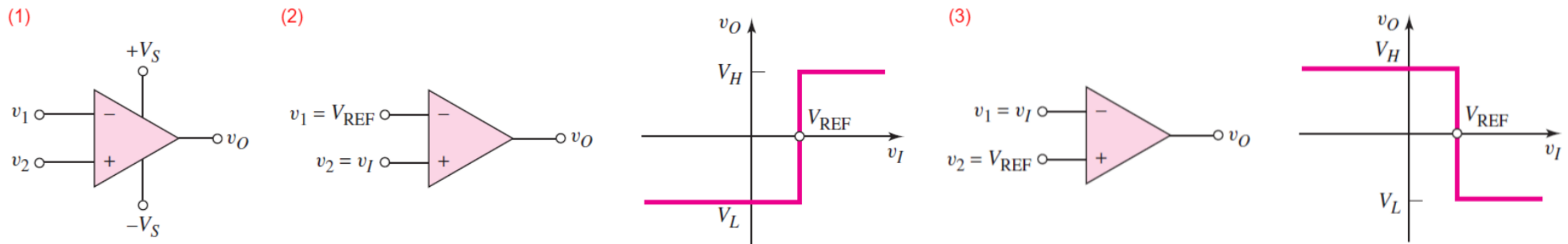


Figure 2: (1) Op-Amp Comparator (2) Noninverting Circuit (3) Inverting Circuit