

CSE251: ELECTRONIC DEVICES AND CIRCUITS

EXPERIMENT 2 :

STUDY OF OP-AMP : INVERTING SUMMING AMPLIFIER , SCHMITT TRIGGER

NAME : ANIKA ISLAM

ID : 21101298

SECTION : 12

GROUP : 03

SEMESTER : SPRING 2023

DATE OF PERFORMANCE : 07/02/2023

DATE OF SUBMISSION : 13/02/2023

3. Add a brief Discussion at the end of the report.

Data Sheet

Task-01:

from multimeter, $v_{I1} = 5V$

from multimeter, $v_{I2} = 1V$

from multimeter, $v_{I3} = 0.5V$

Output Amplitude from equation, $v_O = -(\frac{R_F}{R_1} \times v_{I1} + \frac{R_F}{R_2} \times v_{I2} + \frac{R_F}{R_3} \times v_{I3}) = -6.5V$

Output Amplitude from multimeter, $v_O = -6.75V$

$R_F = 100.1k$; $R_1 = 99.4k$

$R_2 = 99.1k$

$R_3 = 98.9k$

Task-02:

R_1	From Equation, $V_{TH} = -(\frac{R_1}{R_2}) V_S^-$	From Oscilloscope, V_{TH}	From Equation, $V_{TL} = -(\frac{R_1}{R_2}) V_S^+$	From Oscilloscope, V_{TL}
25 k Ω		1.92		-1.88
50 k Ω		2.89		-3.16

$V_S^+ = +5V$

$V_S^- = -5V$

✓
7/2/23

Task-03:

R_1	$p = R_2/R_1$	From Equation, $V_{TH} = 2.5 + \frac{2.5}{p}$	From Oscilloscope, V_{TH}	From Equation, $V_{TL} = 2.5 - \frac{2.5}{p}$	From Oscilloscope, V_{TL}
25 k Ω					
50 k Ω			4.9		

DISCUSSION

For task 1, three $100\text{ k}\Omega$ resistors are connected parallelly to the 2nd pin of op-amp IC. A potentiometer set at $100\text{ k}\Omega$ is connected with the 2nd pin and the 6th pin. 2nd pin is the input and 6th pin is the output. The 3rd pin is connected to the ground. 4th and 5th pin is connected to -15V port of trainer board and set to -8V . 7th pin is connected to 15V port of trainer board and set to 8V . The 1st resistor connected to 2nd pin is connected to 5V port of the trainer board. The 2nd resistor is connected to ^{DC} power supply set at 1V and the 3rd resistor is connected to another DC supply set at 0.5V . Voltage is measured using multimeter, set to measure voltage, in the 6th pin.

For task 2, $100\text{ k}\Omega$ resistor and potentiometer set at $100\text{ k}\Omega$ are connected to the 3rd pin. The 3rd pin is the input. ~~Voltage~~ of 4V voltage and 1kHz frequency are set on the function generator and this is also connected to the 3rd pin. Channel-1 of Oscilloscope is connected to 3rd pin. 2nd pin is grounded. One wiper terminal of potentiometer is connected to 6th pin which is the output. Channel-2 of Oscilloscope is connected to the 6th pin. 4th and 7th pins are connected to -15V and 15V of the trainer board and adjusted to -8V and 8V respectively. The knob of potentiometer is moved to change the resistance to $25\text{ k}\Omega$ and $50\text{ k}\Omega$ and the higher intersection of the two curves is the V_{TH} and the lower intersection is the V_{TN} which is obtained using horizontal cursors in the Oscilloscope.

