

## Experiment-02

### Study of Op-Amp: Inverting Summing Amplifier, Schmitt Trigger

CSE251 - Electronic Devices and Circuits Lab

### Objective

1. To investigate the use of Op-Amp as Inverting Summing Amplifier and Schmitt Trigger

### Equipments

1. Op-Amp (uA741)
2. Resistance (100kΩ)
3. POT (100kΩ)
4. DC power supply
5. Function Generator
6. Trainer Board
7. Breadboard
8. Chords and Wire
9. Digital Multimeter
10. Oscilloscope

### Background Theory

#### Inverting Summing Amplifier

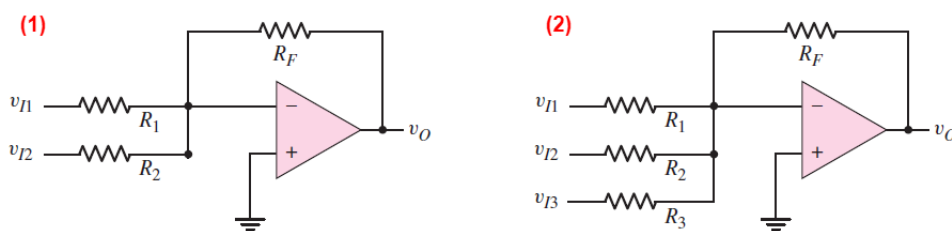


Figure 1: Inverting Summing Amplifier (1) with 2-inputs (2) with 3-inputs

Op-Amps can be used to do weighted summation of multiple input voltages. Figure-1 shows inverting summing amplifier circuits that can do this. The weight of each input voltage during the summing operation can be controlled by the resistances. The circuit does weighted summation and inverts the result at the output. The following equation shows the relationship between the input and output of a 2-input inverting summing amplifier.

$$v_O = -\left(\frac{R_F}{R_1} \times v_{I1} + \frac{R_F}{R_2} \times v_{I2}\right); \text{ where, gain for } v_{I1} = -\frac{R_F}{R_1}, \text{ gain for } v_{I2} = -\frac{R_F}{R_2}$$

We can extend it to as many inputs as we want and the equation will change accordingly. Let's say, we need to add another input  $v_{I3}$ . Then the equation will look like this:

$$v_O = -\left(\frac{R_F}{R_1} \times v_{I1} + \frac{R_F}{R_2} \times v_{I2} + \frac{R_F}{R_3} \times v_{I3}\right)$$

$$\text{where, gain for } v_{I1} = -\frac{R_F}{R_1}, \text{ gain for } v_{I2} = -\frac{R_F}{R_2}, \text{ gain for } v_{I3} = -\frac{R_F}{R_3}$$

## Schmitt Trigger

A Schmitt trigger is a type of comparator circuit that compares an input voltage to a set of threshold values and switches its output based on the comparison. The circuit has two different threshold values, one for switching the output high and one for switching it low. This makes the Schmitt trigger useful in applications where noise or rapid voltage changes need to be filtered out and only clean digital signals are desired. The Schmitt trigger is widely used in digital electronics.

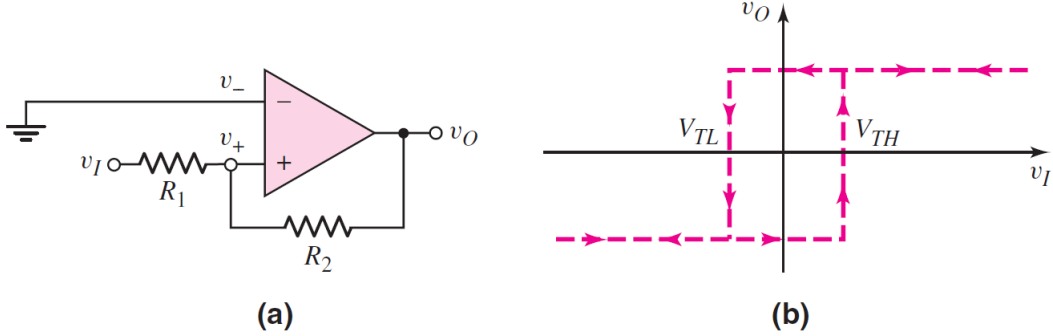


Figure 2: (a) Non-inverting Schmitt trigger circuit and (b) voltage transfer characteristics

Schmitt trigger uses positive feedback mechanism and its threshold voltages depend on the output voltage. Figure-2 shows a non-inverting schmitt trigger circuit and its transfer characteristics. In the circuit, we choose the value of the resistances in such a way that,  $R_2 = pR_1$ .

In a comparator,  $v_O = V_s^+$  when  $v_+ > v_-$ ,  $v_O = V_s^-$  when  $v_- > v_+$  and  $v_O$  transitions from  $V_s^+$  to  $V_s^-$  when  $v_+ = v_-$ . We need to get the value of  $v_I$  for which this transition occurs. Now in this schmitt trigger circuit,

$$\begin{aligned}
 I_{R1} &= I_{R2} \\
 \Rightarrow \frac{v_I - v_+}{R_1} &= \frac{v_+ - v_O}{R_2} \\
 \Rightarrow \frac{v_I - v_+}{R_1} &= \frac{v_+ - v_O}{pR_1} \\
 \Rightarrow v_+ \left(1 + \frac{1}{p}\right) &= v_I + \frac{v_O}{p}
 \end{aligned}$$

In this circuit,  $v_- = 0$ . So, if at any moment,  $v_-$  becomes equal to  $v_+$ , we can write,

$$\begin{aligned}
 v_+ &= 0 \\
 \Rightarrow v_+ \left(1 + \frac{1}{p}\right) &= 0 \\
 \Rightarrow v_I + \frac{v_O}{p} &= 0 \\
 \Rightarrow v_I &= -\frac{v_O}{p}
 \end{aligned}$$

We can conclude that,  $v_+ = v_-$  for  $v_I = -\frac{v_O}{p}$ , which gives us the transition point. If we carefully observe the equation, we see that it depends on  $v_O$ . So, we get 2 transition points,

$$\begin{aligned}
 v_I &= \frac{-V_S^+}{p}, \quad \text{when initially } v_O = V_S^+ \\
 v_I &= \frac{-V_S^-}{p}, \quad \text{when initially } v_O = V_S^-
 \end{aligned}$$

We can say that, these 2 transition points are 2 thresholds where the schmitt trigger changes its output from  $V_S^+$  to  $V_S^-$  or from  $V_S^-$  to  $V_S^+$ . We call them Lower Threshold,  $V_{LH}$  and Higher Threshold,  $V_{TH}$  respectively. Now, we can write  $v_+$  as a function of  $v_I$  and  $v_O$ . Using superposition, we get,

$$v_+ = \left(\frac{R_2}{R_1 + R_2}\right)v_I + \left(\frac{R_1}{R_1 + R_2}\right)v_O$$

If  $v_I$  is negative, and the output is in its low state, then  $v_O = V_S^-$  (assumed to be negative),  $v_+$  is negative, and the output remains in  $V_S^-$ . Transition voltage  $v_I = V_{TH}$  occurs when  $v_+ = 0$  and  $v_O = V_S^-$ , we get,

$$\begin{aligned} R_2 V_{TH} + R_1 V_S^- &= 0 \\ \Rightarrow V_{TH} &= -\left(\frac{R_1}{R_2}\right) V_S^- \end{aligned}$$

Since  $V_S^-$  is negative,  $V_{TH}$  is positive. If we let  $v_I = V_{TH} + \delta$ , where  $\delta$  is a small positive voltage, the input voltage is just greater than the transition/threshold voltage and we get,

$$\begin{aligned} v_+ &= \left(\frac{R_2}{R_1 + R_2}\right) (V_{TH} + \delta) + \left(\frac{R_1}{R_1 + R_2}\right) V_S^- \\ \Rightarrow v_+ &= \left(\frac{R_2}{R_1 + R_2}\right) \left(\frac{-R_1}{R_2}\right) V_S^- + \left(\frac{R_2}{R_1 + R_2}\right) \delta + \left(\frac{R_1}{R_1 + R_2}\right) V_S^- \\ \Rightarrow v_+ &= \left(\frac{R_2}{R_1 + R_2}\right) \delta > 0 \end{aligned}$$

When  $v_+ > 0$ , the output switches to  $V_S^+$ .

The lower threshold voltage  $v_I = V_{TL}$  occurs when  $v_+ = 0$  and  $v_O = V_S^+$ . We can write,

$$\begin{aligned} R_2 V_{TL} + R_1 V_S^+ &= 0 \\ \Rightarrow V_{TL} &= -\left(\frac{R_1}{R_2}\right) V_S^+ \end{aligned}$$

Since  $V_S^+ > 0$ , then  $V_{TL} < 0$ . The complete voltage transfer characteristics are shown in Figure-2(b).

### Schmitt Trigger Circuits with Applied Reference Voltage

Both  $V_{TH}$  and  $V_{TL}$  can be shifted in either a positive or negative direction by applying a reference voltage in the schmitt trigger circuit. The following circuit demonstrates this phenomenon.

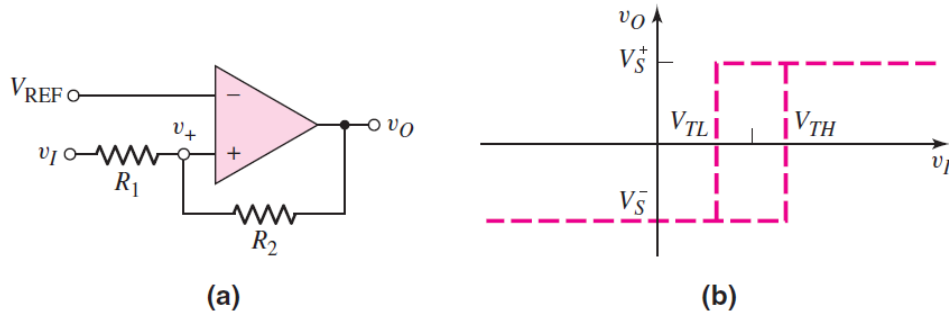


Figure 3: (a) Non-inverting Schmitt trigger circuit with applied reference voltage and (b) voltage transfer characteristics

If we analyze this circuit like the previous one, for transition we get,

$$\begin{aligned} v_+ &= v_- = V_{REF} \\ \Rightarrow v_+ \left(1 + \frac{1}{p}\right) &= V_{REF} \left(1 + \frac{1}{p}\right) \\ \Rightarrow v_I + \frac{v_O}{p} &= V_{REF} \left(1 + \frac{1}{p}\right) \end{aligned}$$

When initially,  $v_O = V_S^-$ ,

$$\begin{aligned} v_I + \frac{V_S^-}{p} &= V_{REF} \left(1 + \frac{1}{p}\right) \\ \Rightarrow v_I = V_{TH} &= V_{REF} \left(1 + \frac{1}{p}\right) - \frac{V_S^-}{p} \end{aligned}$$

When initially,  $v_O = V_S^+$ ,

$$v_I + \frac{V_S^+}{p} = V_{REF}(1 + \frac{1}{p})$$

$$\Rightarrow v_I = V_{TL} = V_{REF}(1 + \frac{1}{p}) - \frac{V_S^+}{p}$$


In this circuit, we will use  $V_{REF} = 2.5$  V,  $V_S^+ = 5$  V and  $V_S^- = 0$  V. So we get,

$$V_{TH} = 2.5 + \frac{2.5}{p} \quad \text{and} \quad V_{TL} = 2.5 - \frac{2.5}{p}$$

So, changing the ratio of  $p = R_2/R_1$  will let us choose our desired value of  $V_{TH}$  and  $V_{TL}$ .

## Task-01: Inverting Summing Amplifier

---

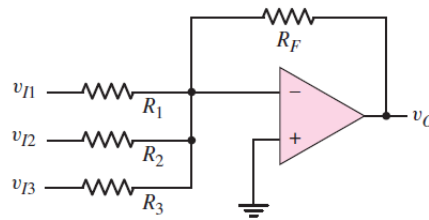


### Procedure

1. Construct the circuit with 3-inputs where the supply voltage  $+V_S$  and  $-V_S$  should be  $+8$  V and  $-8$  V respectively. Use the Trainer board for the supply voltages.
2. Use the DC Power Supply for  $v_{I1} = 0.5$  V,  $v_{I2} = 1$  V and the Trainer Board for  $v_{I3} = 5$  V.
3. Use  $R_1 = 100$  k $\Omega$ ,  $R_2 = 100$  k $\Omega$ ,  $R_3 = 100$  k $\Omega$  and  $R_F = 100$  k $\Omega$ .
4. Use the digital multimeter to measure the output voltage and write down the values according to the data sheet.

## Task-02: Schmitt Trigger


---

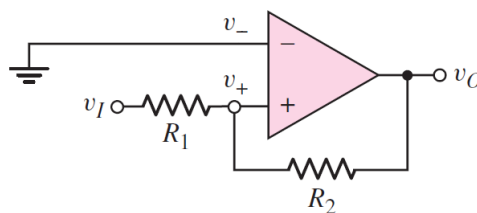

### Procedure

1. Construct the circuit where the supply voltage  $+V_S$  and  $-V_S$  should be  $+5$  V and  $-5$  V respectively. Use the Trainer board for the supply voltages.
2. Use a  $100$  k $\Omega$  POT for  $R_1$ . Use  $R_2 = 100$  k $\Omega$ .
3. Use the Function Generator to generate  $v_I = 8$  V (p-p)  $1$  KHz.
4. Connect the Ch-1 and Ch-2 of the oscilloscope to  $v_I$  and  $v_O$  respectively.
5. Change the value of  $R_1$  (as it is a POT) and observe the output voltage and write down the values according to the data sheet.
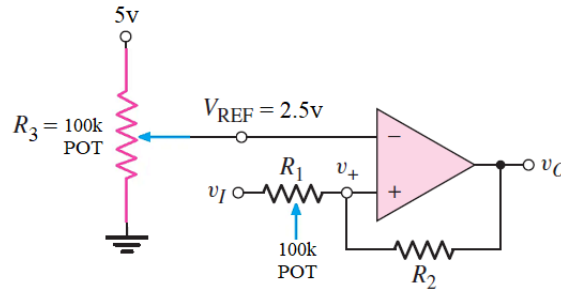
## Task-03: Schmitt Trigger with Applied Reference Voltage



### Procedure

1. Construct the circuit where the supply voltage  $+V_S$  and  $-V_S$  should be  $+5\text{ V}$  and  $0\text{ V}$  respectively. Use the Trainer board for the supply voltages. Use a  $100\text{ k}\Omega$  POT for  $R_1$  and  $R_3$ . Use  $R_2 = 100\text{ k}\Omega$ .
2. Use the Function Generator to generate  $v_I = 8\text{ V}$  (p-p)  $1\text{ KHz}$  and connect the Ch-1 and Ch-2 of the oscilloscope to  $v_I$  and  $v_O$  respectively.
3. Change the value of  $R_3$  (as it is a POT) so that  $V_{REF} = 2.5\text{ V}$  (use multimeter).
4. Change the value of  $R_1$  (as it is a POT) and observe the output voltage and write down the values according to the data sheet.

## Task-04: Report

1. Cover page [include course code, course title, name, student ID, group, semester, date of performance, date of submission]
2. Attach the signed Data Sheet.
3. Add a brief Discussion at the end of the report.

## Data Sheet

### Task-01:

from multimeter,  $v_{I1} =$

from multimeter,  $v_{I2} =$

from multimeter,  $v_{I3} =$

Output Amplitude from equation,  $v_O = -\left(\frac{R_F}{R_1} \times v_{I1} + \frac{R_F}{R_2} \times v_{I2} + \frac{R_F}{R_3} \times v_{I3}\right) =$

Output Amplitude from multimeter,  $v_O =$

### Task-02:

| $R_1$         | From Equation,<br>$V_{TH} = -\left(\frac{R_1}{R_2}\right) V_S^-$ | From Oscilloscope,<br>$V_{TH}$ | From Equation,<br>$V_{TL} = -\left(\frac{R_1}{R_2}\right) V_S^+$ | From Oscilloscope,<br>$V_{TL}$ |
|---------------|--|--------------------------------|--|--------------------------------|
| 25 k $\Omega$ |  |                                |  |                                |
| 50 k $\Omega$ |  |                                |  |                                |

### Task-03:

| $R_1$         | $p = R_2/R_1$ | From Equation,<br>$V_{TH} = 2.5 + \frac{2.5}{p}$ | From Oscilloscope,<br>$V_{TH}$ | From Equation,<br>$V_{TL} = 2.5 - \frac{2.5}{p}$ | From Oscilloscope,<br>$V_{TL}$ |
|---------------|---------------|--|--------------------------------|--|--------------------------------|
| 25 k $\Omega$ |               |  |                                |  |                                |
| 50 k $\Omega$ |               |  |                                |  |                                |